

Fundamentals of EE 3

Chapter 3.1

Transient processes - The Laplace transform

Prof. Dr.-Ing. I. Willms

UNIVERSITÄT
DUISBURG
ESSEN

Fundamentals of EE 3
S. 1

Fachgebiet
Nachrichtentechnische Systeme



3.1.1 Introduction

Use of a complex frequency p for time signals. It applies: $p = \sigma + j\omega$


Thus exponential envelopes are representable for sinusoidal functions in addition to those with constant amplitudes:

Example for RLC resonant circuit:

$$u_1(t) = \text{Re} \{ \hat{u}_1 e^{pt} \}$$

$$u_2(t) = \text{Re} \{ \hat{u}_2 e^{pt} \}$$
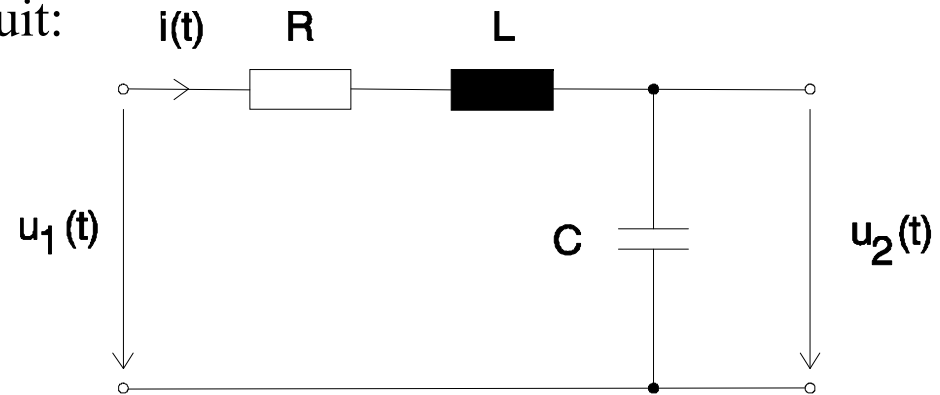
$$i(t) = \text{Re} \{ \hat{i} e^{pt} \}$$



3.1.1 Introduction

A network analysis shows here that it applies:

$$u_1(t) = i(t)R + L \frac{di(t)}{dt} + \frac{1}{C} \int_{-\infty}^t i(z) dz$$
$$\Rightarrow u_1(t) = i(t)R + L \frac{di(t)}{dt} + \frac{1}{C} \int_{-\infty}^0 i(z) dz + \frac{1}{C} \int_0^t i(z) dz \quad \left| \quad u_2(0) = \frac{1}{C} \int_{-\infty}^0 i(z) dz \right.$$

Solution can be achieved by means of:

- solution of the integro-differential equations
- the Laplace transform



3.1.2 Definition of the Laplace transform

An arbitrary function is given: $f(t) = \begin{cases} 0 & \text{for } -\infty \leq t < 0 \\ g(t) & \text{for } 0 < t \leq +\infty \end{cases}$

$f(t)$ exhibits the following characteristics:

- 1) $f(t)$ has only finite jumps in the interval $0 < t_1 \leq t \leq t_2$
- 2) $\int_0^{t_2} f(t) dt$ is limited
- 3) $f(t)$ should drop to zero quickly enough: $\lim_{t \rightarrow \infty} f(t) \rightarrow e^{-\sigma_0 t}$

If these conditions are fulfilled

the Laplace transform of the function $f(t)$ exists:

$$\Rightarrow \mathcal{L}\{f(t)\} = \mathcal{L}\{g(t)\} = \underline{G}(p) = \int_0^{+\infty} g(t)e^{-pt} dt$$



3.1.2 Definition of the Laplace transform

The relation of original signals and corresponding transform is described by the symbol after DOETSCH:

$$g(t) \circ \text{---} \bullet \underline{G}(p) \quad \underline{G}(p) \bullet \text{---} \circ g(t)$$

Relation with Fourier transform is given for:

- a causal time function and at the same time
- a modified time function due to multiplication with $e^{-\sigma t}$

This leads in the integrand of the Fourier Transf. to a term $s(t) \cdot e^{-\sigma t} e^{-j\omega t} = s(t)e^{-pt}$

$$L\{s(t)\} = \int_0^{\infty} s(t) e^{-pt} dt = S(p)$$

$$L^{-1}\{S(p)\} = \lim_{\omega \rightarrow \infty} \frac{1}{2\pi j} \int_{\sigma-j\omega}^{\sigma+j\omega} S(p) e^{pt} dp = s(t)$$



3.1.3 Methods for the determination of the original function from the image function

Direct method:

The original function can be determined according to the relationship:

$$g(t) = \frac{1}{2\pi j} \lim_{\omega \rightarrow \infty} \int_{\sigma - j\omega}^{\sigma + j\omega} \underline{G}(p) e^{pt} dp \quad \text{for } t > 0$$

The use of this formula requires however some knowledge of the function theory.



3.1.3 Methods for the determination of the original function from the image function

Use of transformation tables:

Example: In a network it applies to the transform of the current:

$$\mathcal{L}\{i(t)\} = \frac{U_0}{R} \frac{1}{p(1 + \tau p)} \quad \text{with} \quad \tau = \frac{L}{R}$$

The original function $i(t)$ of the current is looked for.

Solution: From a transformation table one receives:

$$\left(1 - e^{-\frac{t}{a}}\right) \longleftrightarrow \frac{1}{p(1 + ap)}$$

With $a = \tau$ it applies then to the original function: $i(t) = \frac{U_0}{R} \left(1 - e^{-\frac{t}{\tau}}\right)$



3.1.3 Methods for the determination of the original function from the image function

The method of decomposition into partial fractions:

It accepted that itself the image function $\underline{G}(p)$ in a broken rational function:

$$\underline{G}(p) = \frac{\underline{Z}(p)}{\underline{N}(p)}$$

Order of the nominator polynomial $\underline{N}(p) <$ Order of the denominator polynomial

The individual partial fractions have thereby the form:

$$\frac{\underline{A}_v}{(p - p_v)^k} \quad k = 1, 2, 3, \dots$$

Now for each partial fraction if the respective original function is intended, then results in itself as sum of these the original function $g(t)$.



3.1.3 Methods for the determination of the original function from the image function

The Heaviside expansion theorem:

- ➔ Conditions: $\underline{G}(p)$ is a broken rational function,
The denominator degree is higher than the nominator degree,
The denominator polynomial has only n simple zeros ($k = 1$)

$$\text{Thus it applies: } \underline{G}(p) = \frac{\underline{Z}(p)}{\underline{N}(p)} = \sum_{v=1}^n \frac{\underline{A}_v}{p - p_v}$$

$$\longleftrightarrow (p - p_v) \cdot \underline{G}(p) = \frac{(p - p_v) \underline{Z}(p)}{\underline{N}(p)} = (p - p_v) \left(\frac{\underline{A}_1}{p - p_1} + \frac{\underline{A}_2}{p - p_2} + \dots + \frac{\underline{A}_v}{p - p_v} + \dots + \frac{\underline{A}_n}{p - p_n} \right)$$

$$(p - p_v) \cdot \underline{G}(p) = \frac{(p - p_v) \cdot \underline{Z}(p)}{\underline{N}(p)} = \underline{A}_v \quad \text{for limiting with } p \rightarrow p_v$$

3.1.3 Methods for the determination of the original function from the image function

- For further solution the L'Hospital rule must be used (if linear factor form is not given):

$$\underline{A}_v = \lim_{p \rightarrow p_v} \frac{\frac{d}{dp} [(p - p_v) \underline{Z}(p)]}{\frac{d}{dp} [\underline{N}(p)]} = \lim_{p \rightarrow p_v} \frac{\underline{Z}(p) + \overbrace{(p - p_v) \underline{Z}'(p)}^0}{\underline{N}'(p)}$$

Thus it applies:

$$\underline{A}_v = \lim_{p \rightarrow p_v} \frac{\underline{Z}(p)}{\underline{N}'(p)}$$

Because of the correspondence

$$e^{p_v t} \longleftrightarrow \frac{1}{p - p_v}$$

the original function gives:

$$g(t) = \sum_{v=1}^n A_v e^{p_v t}$$

3.1.3 Methods for the determination of the original function from the image function

The modified Heaviside expansion theorem:

In case of a pole at the origin the following applies:

$$\underline{G}(p) = \frac{\underline{Z}_1(p)}{p \cdot \underline{N}_1(p)} \quad \text{with} \quad p_1 = 0$$

For the original function arises then:

$$g(t) = \frac{\underline{Z}_1(0)}{\underline{N}_1(0)} + \sum_{v=2}^n \frac{\underline{Z}_1(p_v)}{p \underline{N}'_1(p_v)} \cdot e^{p_v t}$$

Example: In a network is the image function of a branch current is as follows:

$$\mathcal{L}\{i_z(t)\} = \frac{U}{L} \cdot \frac{p + 1/\tau}{p \left[p^2(1-k^2) + 2p/\tau + 1/\tau^2 \right]}$$



3.1.3 Methods for the determination of the original function from the image function

- Solution:

$$\underline{Z}_1(p) = p + \frac{1}{\tau}$$

$$\underline{N}_1(p) = p^2(1-k^2) + 2\frac{p}{\tau} + \frac{1}{\tau^2} \quad ; \quad \underline{N}'_1(p) = 2\left[p(1-k^2) + \frac{1}{\tau}\right]$$

Thus it applies:

$$i_z(t) = \frac{U}{L} \left[\frac{\frac{1}{\tau}}{\frac{1}{\tau^2}} + \frac{p_2 + \frac{1}{\tau}}{2\left[p_2(1-k^2) + \frac{1}{\tau}\right]} e^{p_2 t} + \frac{p_3 + \frac{1}{\tau}}{2\left[p_3(1-k^2) + \frac{1}{\tau}\right]} e^{p_3 t} \right]$$




Fundamentals of EE 3

Chapter 3.2

Transient processes - Application of the Laplace transform



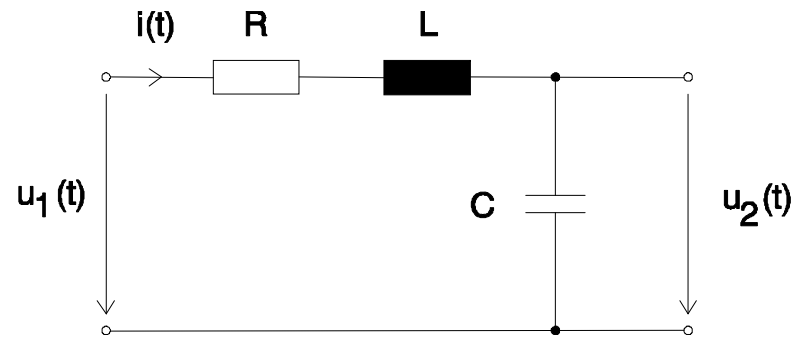3.2. Application of the Laplace transform



$$u_1(t) = i(t)R + L \frac{di(t)}{dt} + \frac{1}{C} \int_{-\infty}^t i(z) dz$$

$$\Rightarrow u_1(t) = i(t)R + L \frac{di(t)}{dt} + \frac{1}{C} \int_{-\infty}^0 i(z) dz + \frac{1}{C} \int_0^t i(z) dz \quad \left| \quad u_2(0) = \frac{1}{C} \int_{-\infty}^0 i(z) dz \right.$$



$$U_1(p) = I(p)R + L[pI(p) - i(0)] + \frac{1}{C} \frac{I(p)}{p} + \frac{u_2(0)}{p}$$

$$= I(p)R + pLI(p) + \frac{1}{pC} I(p) - i(0)L + \frac{u_2(0)}{p}$$



3.2. Application of the Laplace transform

- Dissolve for the transform of current and voltage gives for zero-state condition:

$$U_1(p) = I(p) \cdot (R + pL + 1/pC)$$

$$I(p) = \frac{U_1(p)}{R + pL + 1/pC}$$

$$\Rightarrow i(t) = L^{-1} \left\{ \frac{U_1(p)}{R + pL + 1/pC} \right\}$$

For comparison:

NW-Analyses would have given:

$$\underline{\hat{u}}_1 = R\underline{\hat{i}} + pL\underline{\hat{i}} + \frac{1}{pC}\underline{\hat{i}}$$



3.2. Application of the Laplace transform

Procedure for general solution of the network variables:

1. NW-analysis in the time intervall \rightarrow System of integro-differential equations
2. Laplace transform of the integro-differential equation system after specifying the initial values at $t = 0$ and determination of the Laplace Transforms
3. Dissolution after Laplace transforms of the unknown variables by means of algebra rewriting
4. Inverse transform to the desired variables.



Fundamentals of EE 3

Chapter 3.3


The classical method of directly solving differential equations



3.3.1 Introduction

Repetition to network elements concerning current, voltage, energy and/or instantaneous power $p(t)$:

1) Resistor :

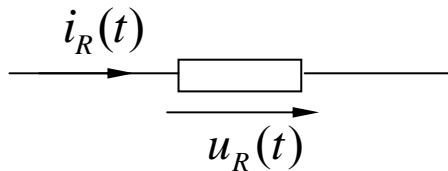


$$u_R(t) = Ri_R(t)$$

$$W = \int p(t)dt = \int u(t)i(t)dt$$



3.3.1 Introduction

2) Coil:

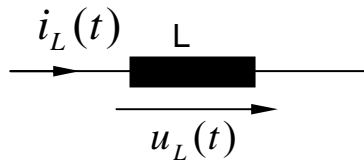


$$u_L(t) = L \frac{di_L(t)}{dt} \quad \text{oder}$$

$$i_L(t) = \frac{1}{L} \int_{-\infty}^t u_L(\tau) d\tau$$

$$W_{\text{magn}} = \int_{-\infty}^t p(\tau) d\tau = \int_{-\infty}^t L \frac{di}{dt} i(t) dt = L \int_0^{i_L(t)} idi = \frac{1}{2} Li_L(t)^2$$

3) Capacitor :

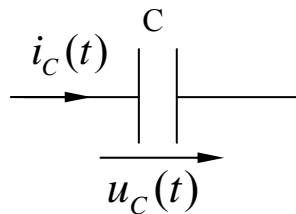

$$u_C(t) = \frac{1}{C} \int_{-\infty}^t i_C(\tau) d\tau$$

$$i_C(t) = C \frac{du_C(t)}{dt}$$


$$W_{\text{el}} = \int_{-\infty}^t p(\tau) d\tau = C \int_0^{u_C(t)} u du = \frac{1}{2} Cu_C(t)^2$$



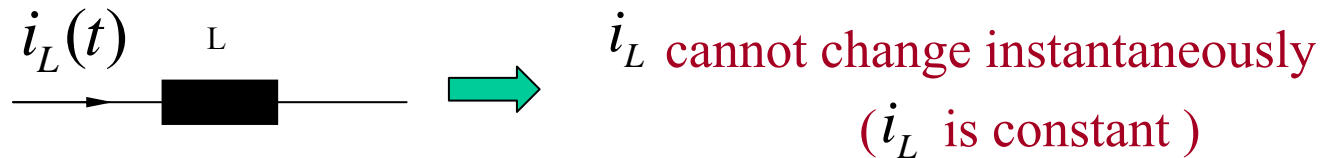
3.3.1 Introduction

In the network only finite voltages and currents are possible.

Thus: No instantaneous change of the energy of these elements is possible



$$i_L(t - \Delta t) = i_L(t + \Delta t) \Big|_{\text{for } \Delta t \rightarrow 0} \quad t = 0 \rightarrow i_L(t = -0) = i_L(t = +0)$$

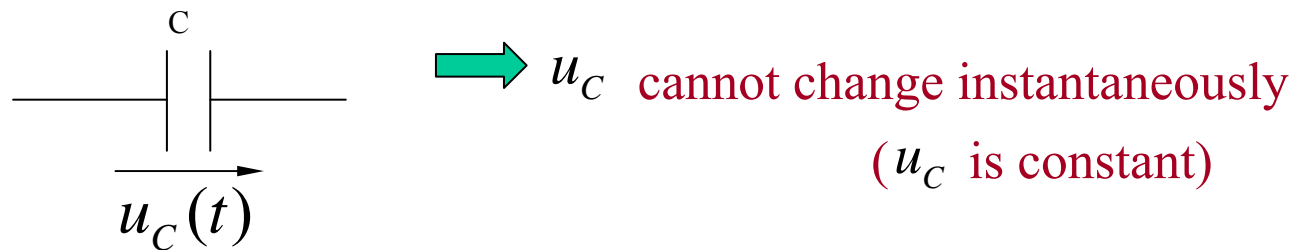

$$u_C(t - \Delta t) = u_C(t + \Delta t) \Big|_{\text{for } \Delta t \rightarrow 0} \quad t = 0 \rightarrow u_C(t = -0) = u_C(t = +0)$$



3.3.2 *The method of the differential equations*

- Kirchhoff's equations lead to differential equations
- These equations have only constant coefficients
- Their solutions provide the desired network variables
- 1. Step: Solution of the system of the homogeneous differential equations
(which represent the natural oscillations of the network)
- 2. Step: Add in each case an individual (particular) solution.

Thus the general solution of the system of the inhomogenous differential equations is obtained:


$$i(t) = i_h(t) + i_p(t) \qquad u(t) = u_h(t) + u_p(t)$$

For a network with DC or constant sinusoidal excitation, the particular describe the steady-state conditions at the time $t \rightarrow \infty$



3.3.2 The method of the differential equations

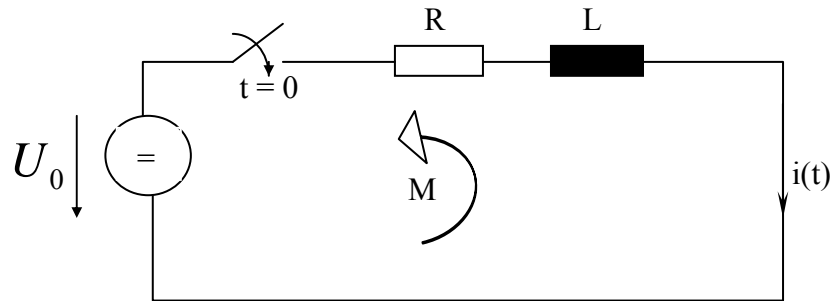Example 1 : Connection of DC voltage to a "RL - circuit".



At the time $t = 0$ the network is connected to a source. The current $i(t)$ is computed with the initial condition:

$$i(t = -0) = 0$$

Solution : For $t \geq 0$ applies:

$$Ri(t) + L \frac{di(t)}{dt} = U_0$$



The differential equation is a usual, linear differential equation of first order with constant coefficients, which is inhomogenous.

3.3.2 The method of the differential equations

A) Solution of the homogeneous differential equation:

$$Ri(t) + L \frac{di(t)}{dt} = 0 \quad \longleftrightarrow \quad \frac{di(t)}{dt} + \frac{R}{L}i(t) = 0$$

On-set: $i_h(t) = Ke^{-\frac{t}{\tau}} \rightarrow \frac{di_h(t)}{dt} = -\frac{K}{\tau}e^{-\frac{t}{\tau}}$

$$\hookrightarrow -\frac{K}{\tau}e^{-\frac{t}{\tau}} + \frac{R}{L}Ke^{-\frac{t}{\tau}} = \left(-\frac{1}{\tau} + \frac{R}{L}\right)Ke^{-\frac{t}{\tau}} = 0 \text{ with } \tau = \frac{L}{R}$$

τ is the time constant of the circuit



3.3.2 The method of the differential equations

$$\frac{di(t)}{dt} + \frac{1}{\tau}i(t) = 0 \quad \longrightarrow \quad i_h(t) = Ke^{-\frac{R}{L}t}$$

B) Individual (particular) solution of the inhomogenous differential equation:

After infinitely long time ($t \rightarrow \infty$) the current of the coil L shows its steady-state value. Then the voltage disappears, i.e. for the current $i(t)$ holds:

$$i_p(t) = \frac{U_0}{R} \neq f(t) \quad \text{for } t \rightarrow \infty$$

This corresponds to the case: $\frac{di_L(t)}{dt} = 0$, d.h. : $u_L = 0$



3.3.2 The method of the differential equations

C) Complete solution:

$$i(t) = i_h(t) + i_p(t) = Ke^{-\frac{R}{L}t} + \frac{U_0}{R}$$

Initial condition: The coil current $i(t = -0) = i(t = +0) = 0$ cannot change instantaneously

$$\leftarrow 0 = \underbrace{Ke^{-\frac{R}{L} \cdot 0}}_1 + \frac{U_0}{R} \rightarrow K = -\frac{U_0}{R}$$

For the current $i(t)$ thus results:



$$i(t) = \frac{U_0}{R} (1 - e^{-\frac{R}{L}t})$$

for $t > 0$


3.3.2 The method of the differential equations

Remarks on the exponential function:

$$f(t) = e^{-\frac{t}{\tau}}$$

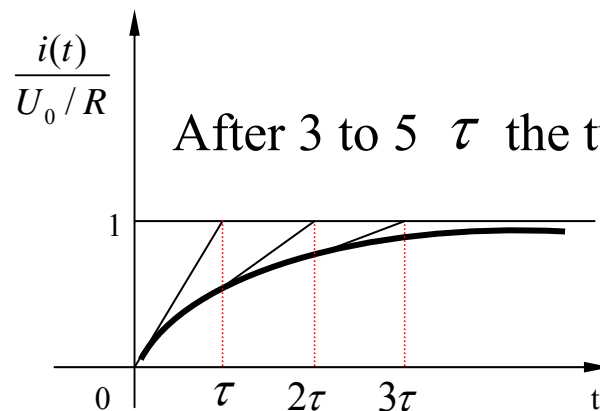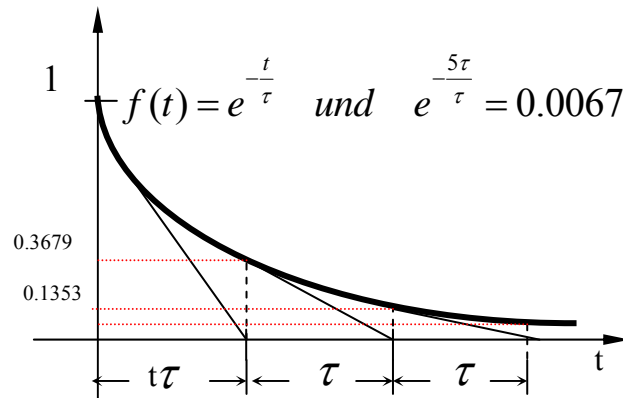

3.3.3 Overview

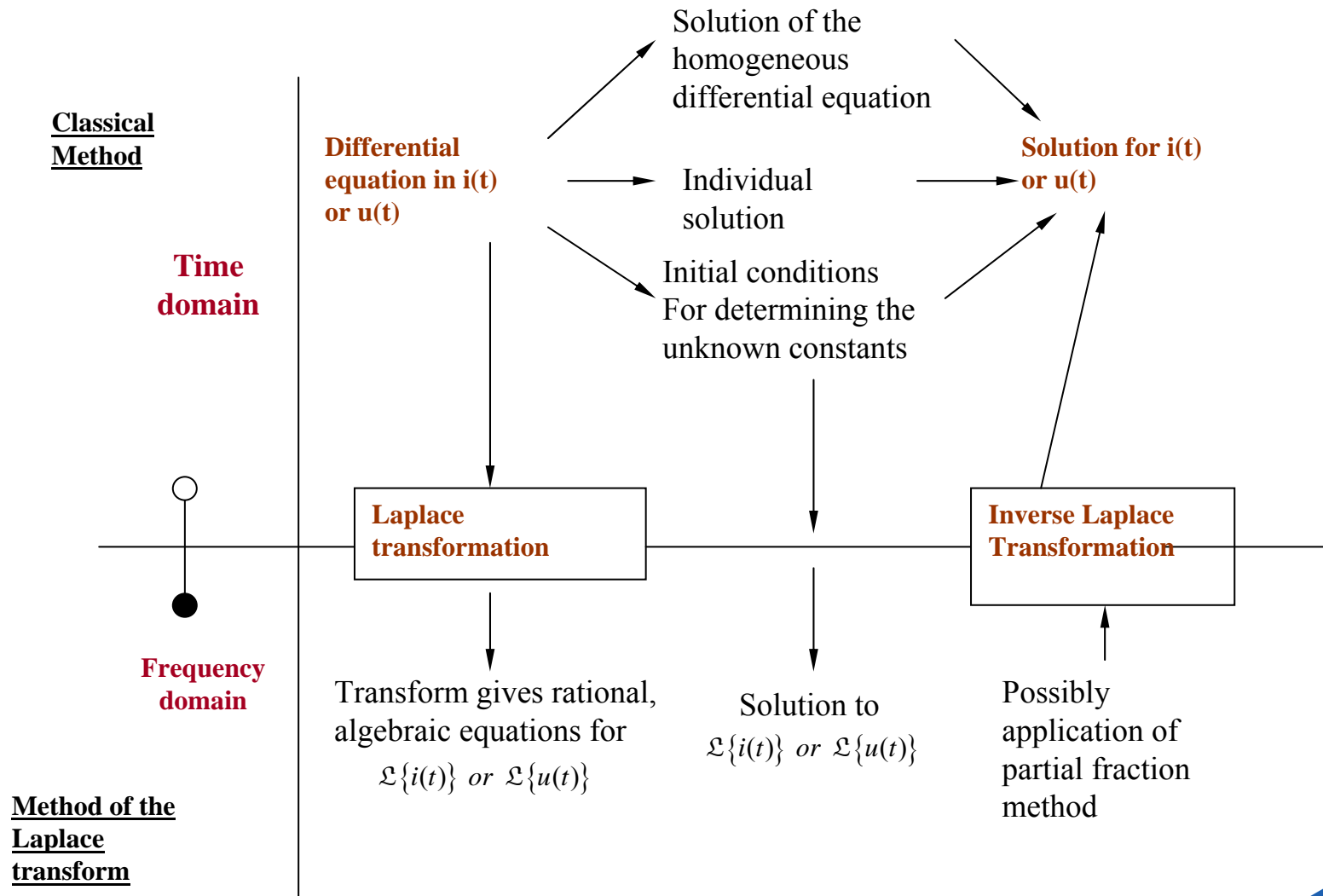

Fundamentals of EE 3


Chapter 3.4

The method of solving differential equations by the Laplace transform



3.4 The method of the Laplace transform

- Example 1:

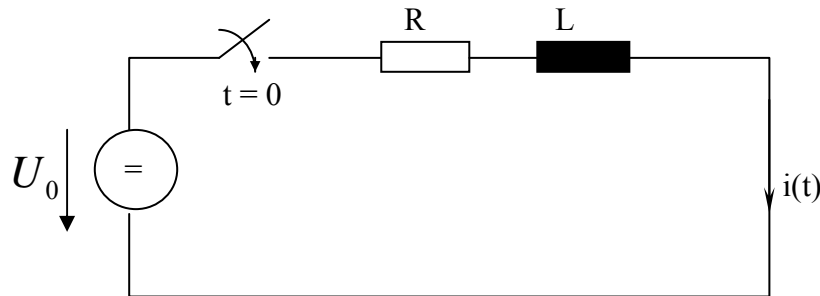

Initial condition: $i(t = -0) = 0$

$$\rightarrow \frac{di(t)}{dt} + \frac{1}{\tau} i(t) = \frac{U_0}{L} \text{ mit } \tau = \frac{L}{R}$$

$$\mathcal{L} \left\{ \frac{di(t)}{dt} \right\} + \frac{1}{\tau} \mathcal{L} \{ i(t) \} = \frac{U_0}{L} \mathcal{L} \{ \varepsilon(t) \}$$

$$p \mathcal{L} \{ i(t) \} - \underbrace{i(0)}_0 + \frac{1}{\tau} \mathcal{L} \{ i(t) \} = \frac{U_0}{L} \frac{1}{p}$$

$$\mathcal{L} \{ i(t) \} \left(p + \frac{1}{\tau} \right) = \frac{U_0}{L} \frac{1}{p}$$



$$\mathcal{L} \{ i(t) \} = \frac{U_0}{L} \frac{1}{p(p + 1/\tau)}$$

3.4 The method of the Laplace transform

The inverse transform can be performed by means of the modified Heaviside` theorem:

$$\mathcal{L}^{-1} \left\{ \underline{I}(p) = \frac{\underline{Z}_1(p)}{p\underline{N}_1(p)} \right\} = i(t) = \frac{\underline{Z}_1(0)}{\underline{N}_1(0)} + \sum_{v=2}^n \frac{\underline{Z}_1(p_v)}{p_v \underline{N}'_1(p_v)} e^{p_v t} \quad \text{with} \quad p_1 = 0 \text{ und } n = 2$$

Thus applies:

$$\underline{Z}_1(p) = \frac{U_0}{L}, \quad \underline{N}_1(p) = p + \frac{1}{\tau}, \quad p_2 = -\frac{1}{\tau}, \quad \underline{N}'_1(p) = 1$$

This gives for the current $i(t)$:

$$i(t) = \frac{U_0}{L} \left[\frac{1}{1/\tau} + \frac{1}{-1/\tau} e^{-\frac{t}{\tau}} \right] = \frac{U_0}{L} \tau \left(1 - e^{-\frac{t}{\tau}} \right) \quad \text{with} \quad \tau = \frac{L}{R}$$

$$i(t) = \frac{U_0}{R} (1 - e^{-\frac{t}{\tau}}) \quad \text{for } t > 0$$



3.4 The method of the Laplace transform

For the inverse transform also the convolution theorem might have been used:

$$\underline{G}_1(p) \cdot \underline{G}_2(p) = \mathcal{L}\{g_1(t) * g_2(t)\} \quad g_2(t) * g_1(t) = \int_0^t g_2(x)g_1(t-x)dx = \int_0^t g_1(x)g_2(t-x)dx$$

$$\mathcal{L}^{-1}\left\{\frac{1}{p}\right\} = 1 \text{ for } t \geq 0 \quad \text{and} \quad \mathcal{L}^{-1}\left\{\frac{1}{p + 1/\tau}\right\} = e^{-\frac{t}{\tau}}$$


Thus it follows:

$$\begin{aligned} \mathcal{L}^{-1}\{i(t)\} &= \mathcal{L}^{-1}\left\{\frac{U_0}{L} \frac{1}{p} \cdot \frac{1}{(p + 1/\tau)}\right\} \\ &= \frac{U_0}{L} \int_0^t 1 \cdot e^{-\frac{x}{\tau}} dx = \frac{U_0}{L} \left[\frac{e^{-\frac{x}{\tau}}}{-\frac{1}{\tau}} \right]_0^t = \frac{U_0}{L} (-\tau) \left(e^{-\frac{t}{\tau}} - 1 \right) \\ &= \frac{U_0}{R} (1 - e^{-\frac{t}{\tau}}) \end{aligned}$$



3.4 The method of the Laplace transform

Example 2:

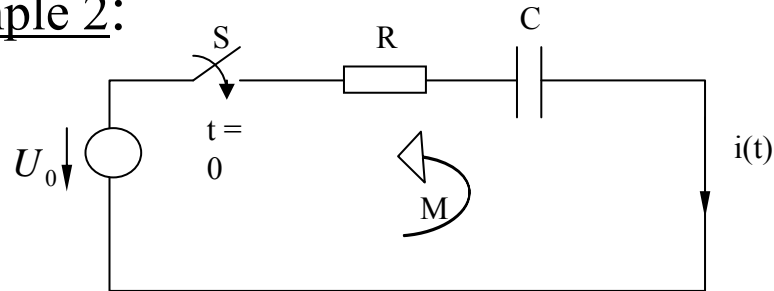

At $t = 0$ the capacitor is charged to Q_0

1) General relations:

$$Ri(t) + \frac{Q(t)}{C} = U_0 \quad \text{mit} \quad Q(t) = Q_0 + \int_0^t i(x) dx$$

$$i(t)R + \frac{Q_0 + \int_0^t i(x) dx}{C} = U_0$$

$$\rightarrow i(t) + \frac{1}{RC} \int_0^t i(x) dx = \frac{U_0}{R} - \frac{Q_0}{RC}$$

3.4 The method of the Laplace transform

2) Solution with the Laplace transform:

$$i(t) + \frac{1}{RC} \int_0^t i(x) dx = \frac{U_0}{R} - \frac{Q_0}{RC}$$

$$\mathcal{L}\{i(t)\} + \frac{1}{RC} \underbrace{\frac{1}{p} \mathcal{L}\{i(t)\}}_{\text{Integration theorem}} = \left(\frac{U_0}{R} - \frac{Q_0}{RC} \right) \mathcal{L}\{\varepsilon(t)\}$$


$$\mathcal{L}\{i(t)\} \left(1 + \frac{1}{RCp} \right) = \left(\frac{U_0}{R} - \frac{Q_0}{RC} \right) \frac{1}{p}$$

$$\mathcal{L}\{i(t)\} = \left(\frac{U_0}{R} - \frac{Q_0}{RC} \right) \frac{RCp}{1+RCp} \frac{1}{p} = \left(\frac{U_0}{R} - \frac{Q_0}{RC} \right) \underbrace{\frac{1}{\frac{1}{RC} + p}}_{\text{Attenuation theorem}}$$

$$i(t) = \left(\frac{U_0}{R} - \frac{Q_0}{RC} \right) e^{-t/RC}$$


for $t > 0$ also $\tau = RC$

Diagram of the results:

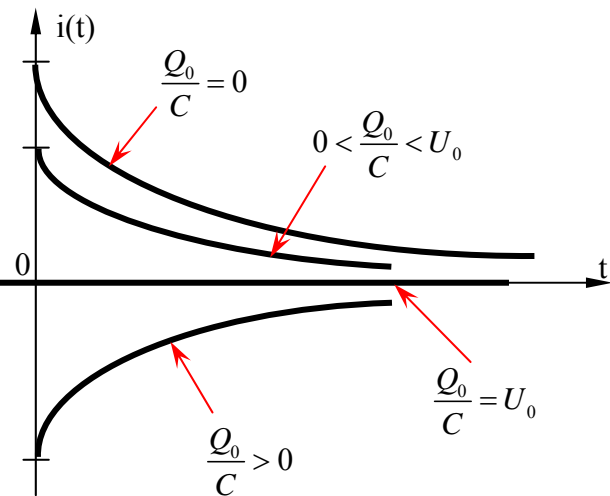

3.4 The method of the Laplace transform

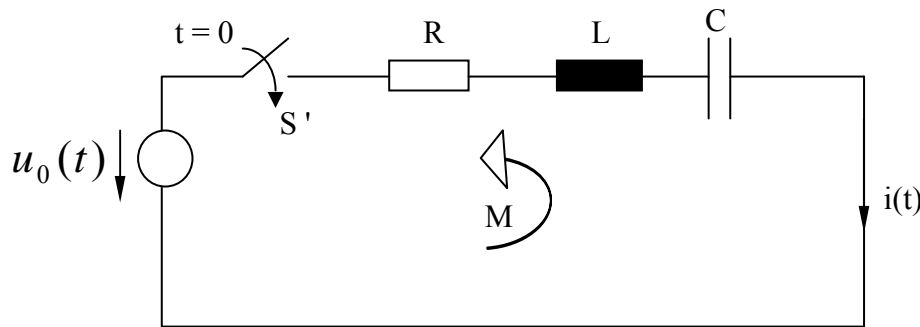Example 3 : In this example a series resonant circuit is connected to a source, with cases a, b and c by an ideal switch S:



a) AC voltage: $u_0(t) = \hat{u}_0 \cos(\omega t + \varphi_u)$

b) DC voltage: $u_0(t) = U_0$

c) Mixed case: $u_0(t) = U_0 + \hat{u}_0 \cos(\omega t + \varphi_u)$

Desired for all 3 cases: $i(t)$ for $t > 0$

0) General relations



The loop equation reads:

$$R \cdot i(t) + L \frac{di(t)}{dt} + u_C(t) = u_0(t) \quad \text{and also} \quad i(t) = C \frac{du_C(t)}{dt} \quad \text{applies.}$$

$$RC \frac{du_C(t)}{dt} + LC \frac{d^2u_C(t)}{dt^2} + u_C(t) = u_0(t)$$

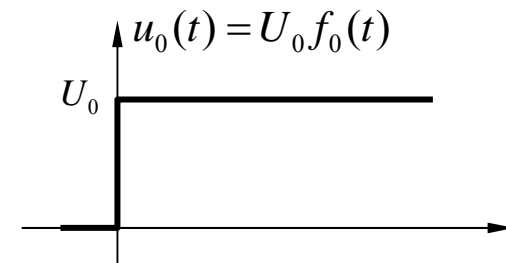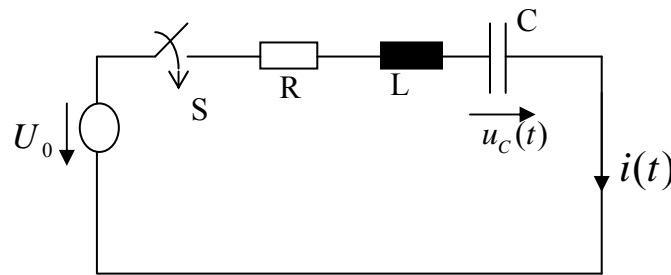3.4 The method of the Laplace transform

- Solution for case 3 ($D < 1$) and source case b) (DC source)



3.4 The method of the Laplace transform

- Solution by means of the Laplace Transform for case 3 ($D < 1$) and source case b) (DC source)

The inhomogenous differential equation is subjected to the Laplace Transform:

$$\frac{d^2 u_c(t)}{dt^2} + 2\omega_0 D \frac{du_c(t)}{dt} + \omega_0^2 u_c(t) = \omega_0^2 U_0 \quad \text{for } t > 0$$



$$p^2 \mathcal{L}\{u_c(t)\} - pu_c(0) - u'_c(0) + 2\omega_0 D [p \mathcal{L}\{u_c(t)\} - u_c(0)] + \omega_0^2 \mathcal{L}\{u_c(t)\} = \frac{\omega_0^2 U_0}{p}$$

With the initial conditions $u_c(0) = 0$ und $u'_c(0) = 0$

it follows:

$$p^2 \mathcal{L}\{u_c(t)\} + 2\omega_0 D p \mathcal{L}\{u_c(t)\} + \omega_0^2 \mathcal{L}\{u_c(t)\} = \frac{\omega_0^2 U_0}{p}$$



3.4 The method of the Laplace transform

Thus it applies to the Laplace transform of $u_C(t)$:

$$\mathcal{L}\{u_C(t)\} = \frac{\omega_0^2 U_0}{p(p^2 + 2\omega_0 D p + \omega_0^2)}$$

The original function can be obtained using the modified theorem of Heaviside:

$$\mathcal{L}\{u_C(t)\} = \frac{\underline{Z}_1(p)}{p\underline{N}_1(p)} \quad \text{with} \quad \underline{Z}_1(p) = \omega_0^2 U_0 \quad , \quad \underline{N}_1(p) = p^2 + 2\omega_0 D p + \omega_0^2$$

$$\frac{d\underline{N}_1(p)}{dp} = 2p + 2\omega_0 D \quad , \quad p_1 = 0, p_2 = \omega_0(-D + j\sqrt{1-D^2})$$

Thus the original function results to:

$$p_3 = \omega_0(-D - j\sqrt{1-D^2})$$


$$u_C(t) = \frac{\underline{Z}_1(0)}{\underline{N}_1(0)} + \sum_{v=2}^3 \frac{\underline{Z}_1(p_v)}{p_v \underline{N}'_1(p_v)} \cdot e^{p_v t} = \frac{\omega_0^2 U_0}{\omega_0^2} + \frac{\omega_0^2 U_0}{p_2 2(p_2 + \omega_0 D)} e^{p_2 t} + \frac{\omega_0^2 U_0}{p_3 2(p_3 + \omega_0 D)} e^{p_3 t}$$



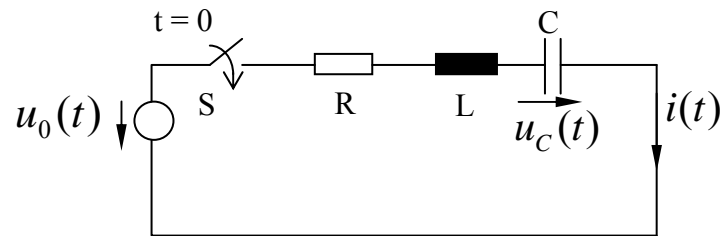3.4 The method of the Laplace transform

- Solution for case 3 ($D < 1$) and source case a) (AC source)

Here only the case of conjugated complex poles (i.e. $D < 1$) is dealt with. For the inhomogenous differential equation then holds:



$$\frac{d^2 u_C(t)}{dt^2} + 2\omega_0 D \frac{du_C(t)}{dt} + \omega_0^2 u_C(t) = \omega_0^2 u_0(t)$$

$$\text{for } t > 0, \text{ also } u_0(t) = \hat{u}_0 \cos(\omega t + \varphi_u)$$

3.4 The method of the Laplace transform

- Solution by means of the Laplace transform for case 3 ($D < 1$) and source case a) (AC source)

Following is the differential equation for $u_c(t)$:

$$\frac{d^2 u_c(t)}{dt^2} + 2\omega_0 D \frac{du_c(t)}{dt} + \omega_0^2 u_c(t) = \omega_0^2 u_0(t)$$

After Laplace transforming of this equation it results:

$$p^2 \mathcal{L}\{u_c(t)\} - pu_c(0) - u_c'(0) + 2\omega_0 D [p \mathcal{L}\{u_c(t)\} - u_c(0)] + \omega_0^2 \mathcal{L}\{u_c(t)\} = \omega_0^2 \mathcal{L}\{u_0(t)\}$$

With the initial conditions: $u_c(0) = 0$ und $u_c'(0) = 0$ it follows:

$$\underline{p}^2 \mathcal{L}\{u_c(t)\} + 2\omega_0 D [\underline{p} \mathcal{L}\{u_c(t)\}] + \omega_0^2 \mathcal{L}\{u_c(t)\} = \omega_0^2 \mathcal{L}\{u_0(t)\}$$



3.4 The method of the Laplace transform

Thus it applies to the image function of $u_c(t)$:

$$\mathcal{L}\{u_c(t)\} = \frac{\omega_0^2 \mathcal{L}\{u_0(t)\}}{p^2 + 2\omega_0 Dp + \omega_0^2}$$

Concerning the source it holds:

$$\mathcal{L}\{u_0(t)\} = \mathcal{L}\{\hat{u}_0 \cos(\omega t + \varphi_u)\} = \hat{u}_0 \frac{p \cos \varphi_u - \omega \sin \varphi_u}{p^2 + \omega^2}$$

Combining the equations given above leads then to:

$$\mathcal{L}\{u_c(t)\} = \hat{u}_0 \omega_0^2 \frac{p \cos \varphi_u - \omega \sin \varphi_u}{(p^2 + \omega^2)(p^2 + 2\omega_0 Dp + \omega_0^2)}$$



3.4 The method of the Laplace transform

The image function must then be back-transformed then into the original domain e.g. with help of the method of the decomposition into partial fractions. Here it applies:

$$\mathcal{L}\{u_c(t)\} = \frac{\underline{Z}(p)}{\underline{N}(p)} \quad \begin{cases} \text{with } \underline{Z}(p) = \hat{u}_0 \omega_0 (p \cos \varphi_u - \omega \sin \varphi_u) \\ \text{and } \underline{N}(p) = (p^2 + \omega^2)(p^2 + 2\omega_0 D p + \omega_0^2) \end{cases}$$

Due to the periodic case ($D < 1$) it applies:

$$p_1 = j\omega, \quad p_2 = -j\omega$$

$$p_{3,4} = \sigma \pm j\omega_1 = \omega_0(-D \pm j\sqrt{1-D^2})$$

For the first derivative of the denominator it applies:

$$\frac{d\underline{N}(p)}{dp} = 4p^3 + 6\omega_0 D p^2 + 2(\omega_0^2 + \omega^2)p + 2\omega_0 D \omega^2$$



3.4 The method of the Laplace transform

Thus finally for the original function holds:

$$u_c(t) = \hat{u}_0 \omega_0^2 \left\{ \frac{j\omega \cos \varphi_u - \omega \sin \varphi_u}{4(j\omega)^3 + 6\omega_0 D(j\omega)^2 + 2(\omega_0^2 + \omega^2)j\omega} e^{j\omega t} + \frac{-j\omega \cos \varphi_u - \omega \sin \varphi_u}{4(-j\omega)^3 + 6\omega_0 D(-j\omega)^2 + 2(\omega_0^2 + \omega^2)(-j\omega)} e^{-j\omega t} \right. \\ \left. + \frac{p_1 \cos \varphi_u - \omega \sin \varphi_u}{4p_1^3 + 6\omega_0 D p_1^2 + 2(\omega_0^2 + \omega^2)p_1 + 2\omega_0 D \omega^2} e^{p_1 t} + \frac{p_2 \cos \varphi_u - \omega \sin \varphi_u}{4p_2^3 + 6\omega_0 D p_2^2 + 2(\omega_0^2 + \omega^2)p_2 + 2\omega_0 D \omega^2} e^{p_2 t} \right\}$$

Final problem:

Further simplification to real values is quite complicated !

