

Network Theory 1

Analoge Netzwerke

Prof. Dr.-Ing. Ingolf Willms

and

Prof. Dr.-Ing. Peter Laws

Prof. Dr.-Ing. I. Willms

UNIVERSITÄT
DUISBURG
ESSEN

Network Theory 1

S. 1

Fachgebiet
Nachrichtentechnische Systeme



Chapter 2


Characteristics and realization of passive two-terminal network function

2.1 Passive two-terminal network functions and their properties



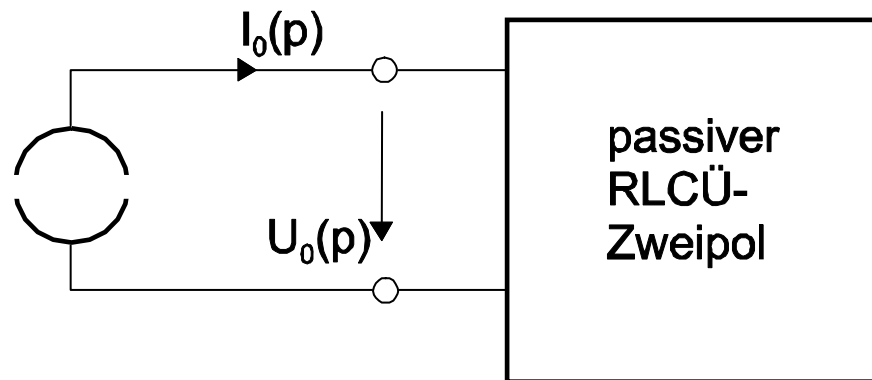2.1.1 The passive RLC two-terminal network function

A passive RLC two-terminal network is stimulated with the current $i_0(t)$:



$$u_0(t) \text{ --- } L \text{ --- } \bullet U_0(p)$$

$$i_0(t) \text{ --- } L \text{ --- } \bullet I_0(p)$$

2.1.1 The passive RLC two-terminal network function

Relationship of a number of w Ohm resistances and the currents:

$$U_w(p) = R_w \cdot I_w(p) \quad \text{with } R_w > 0 \text{ and } w = 1 \quad [1] \quad A$$

Relationship of i inductance and the currents:

$$U_i(p) = pL_i \cdot I_i(p) \quad \text{with } L_i > 0 \text{ and } i = (A+1) \quad [1] \quad B$$

Relationship of k capacitors and the currents:

$$U_k(p) = \frac{1}{pC_k} \cdot I_k(p) \quad \text{with } C_k > 0 \text{ and } k = (B+1) \quad [1] \quad D$$

Here the indices w , i and k just count all passive components.



2.1.1 The passive RLC two-terminal network function

Relation of the primary and secondary ideal transformer parts:

$$U_{\mu+1}(p) = \ddot{u}_{\mu} \cdot U_{\mu}(p) \quad \text{with } \mu = (D+1) \quad [2] \quad E$$

$$I_{\mu+1}(p) = -\frac{1}{\ddot{u}_{\mu}} \cdot I_{\mu}(p) \quad \text{with } \ddot{u}_{\mu} = \frac{w_{\mu+1}}{w_{\mu}} \quad \text{where } \ddot{u}_{\mu} : \text{transformation constant}$$

The number of indicated branches thus is: $\longrightarrow Z = E + 2$



2.1.1 The passive RLC two-terminal network function

With Tellegen's theorem in total Z addends result:

$$\sum_w U_w(p) \cdot I_w^*(p) + \sum_i U_i(p) \cdot I_i^*(p) + \sum_k U_k(p) \cdot I_k^*(p) \\ + \sum_\mu \{U_\mu(p) \cdot I_\mu^*(p) + U_{\mu+1}(p) \cdot I_{\mu+1}^*(p)\} - U_0(p) \cdot I_0^*(p) = 0$$

- The first sum with index w covers \longrightarrow all branches of resistances
- The second sum with index i covers \longrightarrow all branches of inductances
- The 3rd sum with index k covers \longrightarrow all branches of capacitors
- The 4th sum with index μ covers \longrightarrow all branches with ideal transformers
- The minus sign of the last sum \longrightarrow due to the different directions of supply currents and voltages



2.1.1 The passive RLC two-terminal network function

Substitution of voltages by currents in the equations given above leads to:

$$U_0(p) \cdot I_0^*(p) = \sum_w R_w(p) \cdot I_w(p) \cdot I_w^*(p) \\ + \sum_i p \cdot L_i \cdot I_i(p) \cdot I_i^*(p) + \sum_k \frac{1}{p \cdot C_k} \cdot I_k(p) \cdot I_k^*(p)$$

→ The transformers contained in the two-terminal network and their transformer constants \ddot{u}_μ do not have influence on $U_0(p) \cdot I_0^*(p)$ and thus are not part of the sum due to:

$$U_\mu(p) \cdot I_\mu^*(p) + U_{\mu+1}(p) \cdot I_{\mu+1}^*(p) = \\ U_\mu(p) \cdot I_\mu^*(p) + \ddot{u}_\mu U_\mu(p) \cdot \left(-\frac{1}{\ddot{u}_\mu}\right) I_\mu^*(p) = 0$$



2.1.1 The passive RLC two-terminal network function

Division on both sides of the previous equation by

$$I_0(p) \cdot I_0^*(p) = |I_0(p)|^2$$

then gives the following result:

$$\begin{aligned} \frac{U_0(p)I_0^*(p)}{|I_0(p)|^2} &= \frac{U_0(p)}{I_0(p)} = Z(p) \\ &= \sum_w R_w(p) \cdot \frac{|I_w(p)|^2}{|I_0(p)|^2} + p \cdot \sum_i L_i \cdot \frac{|I_i(p)|^2}{|I_0(p)|^2} + \frac{1}{p} \cdot \sum_k \frac{1}{C_k} \cdot \frac{|I_k(p)|^2}{|I_0(p)|^2} \end{aligned}$$



2.1.1 The passive RLC two-terminal network function

After introduction of Brune's pseudo energy functions F , T and V in the equation

$$Z(p) = \sum_w R_w(p) \cdot \frac{|I_w(p)|^2}{|I_0(p)|^2} + p \cdot \sum_i L_i \cdot \frac{|I_i(p)|^2}{|I_0(p)|^2} + \frac{1}{p} \cdot \sum_k \frac{1}{C_k} \cdot \frac{|I_k(p)|^2}{|I_0(p)|^2}$$

with the definitions $F_Z(p) = \sum_w R_w \cdot \frac{|I_w(p)|^2}{|I_0(p)|^2}$ and

$$V_Z(p) = \sum_k \frac{1}{C_k} \cdot \frac{|I_k(p)|^2}{|I_0(p)|^2} \quad T_Z(p) = \sum_i L_i \cdot \frac{|I_i(p)|^2}{|I_0(p)|^2}$$

for all real and positive p it results: a) All pseudo energy functions are positive

$$\text{b) } Z(p) = F_Z(p) + p \cdot T_Z(p) + \frac{1}{p} V_Z(p)$$



2.1.1 The passive RLC two-terminal network function

Replacing p with $(\sigma + j\omega)$ leads to:

$$Z(p) = F_Z(p) + \sigma \cdot T_Z(p) + \frac{\sigma}{\sigma^2 + \omega^2} V_Z(p) + j\omega \cdot \left(T_Z(p) - \frac{1}{\sigma^2 + \omega^2} \cdot V_Z(p) \right)$$

or:

$$\operatorname{Re}\{Z(p)\} = F_Z(p) + \sigma \cdot T_Z(p) + \frac{\sigma}{\sigma^2 + \omega^2} V_Z(p)$$

$$\operatorname{Im}\{Z(p)\} = \omega \cdot \left(T_Z(p) - \frac{1}{\sigma^2 + \omega^2} \cdot V_Z(p) \right)$$



2.1.1 The passive RLC two-terminal network function

Discussion of the result:

$\operatorname{Re}\{Z(p)\} > 0 \quad \forall \operatorname{Re}\{p\} = \sigma > 0$ This is called " $Z(p)$ is positive in p "
(a positive nonzero real value of p gives a positive nonzero real value of $Z(p)$)

Note: $Z(p)$ thus has no zeros in the right open p -plane!

$\operatorname{Re}\{Z(j\omega)\} \geq 0 \quad \forall \omega$ due to $\sigma = 0$

Examining the case of $\omega = 0$, one gets:

$$\operatorname{Re}\{Z(\sigma)\} = F_Z(\sigma) + \sigma \cdot T_Z(\sigma) + \frac{1}{\sigma} V_Z(\sigma)$$

$$\operatorname{Im}\{Z(\sigma)\} = 0$$

This is called " $Z(p)$ is real in p " (a real p value gives a real $Z(p)$ value).



2.1.1 The passive RLC two-terminal network function

For the admittance function of the two-terminal network

$$Y(p) = \frac{I_0(p)}{U_0(p)}$$

it also can be shown that the same properties as for the impedance functions hold.

Thus also $Y(p)$ is positive and real in p .

Due to $\operatorname{Re}\{Z(p)\} > 0 \quad \forall \operatorname{Re}\{p\} > 0$ in combination with $Y(p) = 1/Z(p)$ in the right open p -plane (defined by $\operatorname{Re}\{p\} > 0$) it holds:

$Z(p)$ and $Y(p)$ have no zeros and no poles in the right open p -plane!

So both impedance function $Z(p)$ and the admittance function $Y(p)$ of a passive RLCÜ two-terminal network are positive and real in p .

This is important for realizing circuits.



2.1.2 The passive LC two-terminal network function



2.1.2 The passive LC two-terminal network function

A passive lossless LC two-terminal network contains no Ohm's resistances:

$$\longrightarrow F_z(p) = 0 \quad \text{because of } R_w = 0 \quad \forall w$$

Therefore the impedance function results to:

$$Z(p) = \sigma \cdot T_z(p) + \frac{\sigma}{\sigma^2 + \omega^2} V_z(p) + j\omega \cdot \left(T_z(p) - \frac{1}{\sigma^2 + \omega^2} \cdot V_z(p) \right)$$

with

$$\operatorname{Re}\{Z(p)\} = \sigma \cdot T_z(p) + \frac{\sigma}{\sigma^2 + \omega^2} V_z(p) = 0 \quad \text{only for } \sigma = 0$$

$$\operatorname{Im}\{Z(p)\} = \omega \cdot \left(T_z(p) - \frac{1}{\sigma^2 + \omega^2} \cdot V_z(p) \right)$$



2.1.2 The passive LC two-terminal network function

Now the conditions for zeros of $Z(p)$ are considered.

Note the following conditions for any zero:

$Z(p) = 0$ only holds if both $Re\{Z(p)\} = 0$ and $Im\{Z(p)\} = 0$ hold.

The real part $Re\{Z(p)\}$ as shown before can only be zero on the $j\omega$ -axis.

As specified in the previous slide in general it holds:

$$Z(p) = \sigma \cdot T_Z(p) + \frac{\sigma}{\sigma^2 + \omega^2} V_Z(p) + j\omega \cdot \left(T_Z(p) - \frac{1}{\sigma^2 + \omega^2} \cdot V_Z(p) \right)$$

Therefore, considering $Re\{Z(p)\}$ it holds:

Zeros of $Z(p)$ can lie exclusively on the $j\omega$ – axis of the p -plane



2.1.2 The passive LC two-terminal network function

In addition the following can be shown:

- $Z(p)$ always is imaginary for imaginary p values.
- As $Z(p)$ is the inverse of $Y(p)$ also this function $Y(p)$ is imaginary for imaginary p values.



2.1.2 The passive LC two-terminal network function

The partial fraction representation of $Z(p)$ and/or $Y(p)$:

$$Z(p) = \frac{A_0}{p} + \sum_{\nu=1}^N \frac{2 \cdot A_\nu \cdot p}{p^2 + \omega_{\infty\nu}^2} + A_\infty \cdot p \quad \text{with } A_0, A_\nu, A_\infty : \text{real and positive}$$

$$Y(p) = \frac{B_0}{p} + \sum_{\mu=1}^M \frac{2 \cdot B_\mu \cdot p}{p^2 + \omega_{\infty\mu}^2} + B_\infty \cdot p \quad \text{with } B_0, B_\mu, B_\infty : \text{real and positive}$$

With these formulas one can determine the partial fractions development coefficients of any given impedance or admittance function.

When evaluating $Z(p)$ or $Y(p)$ at the poles locations it can be seen that only real and positive development coefficients ensure that these functions are positive and real in p , i.e. $Z(p)$ and $Y(p)$ are real and positive for any real and positive p including the pole locations.



2.1.2 The passive LC two-terminal network function

Coefficients of impedance function

$Z(p)$:

$$A_0 = \lim_{p \rightarrow 0} \{ p \cdot Z(p) \}$$

$$A_\nu = \frac{1}{2} \cdot \lim_{p^2 \rightarrow -\omega_{\infty \nu}^2} \left\{ \frac{Z(p)}{p} \cdot (p^2 + \omega_{\infty \nu}^2) \right\}$$

$$A_\infty = \lim_{p \rightarrow \infty} \left\{ \frac{Z(p)}{p} \right\}$$

Coefficients of admittance function

$Y(p)$:

$$B_0 = \lim_{p \rightarrow 0} \{ p \cdot Y(p) \}$$

$$B_\mu = \frac{1}{2} \cdot \lim_{p^2 \rightarrow -\omega_{\infty \mu}^2} \left\{ \frac{Y(p)}{p} \cdot (p^2 + \omega_{\infty \mu}^2) \right\}$$

$$B_\infty = \lim_{p \rightarrow \infty} \left\{ \frac{Y(p)}{p} \right\}$$



2.1.2 The passive LC two-terminal network function

Summary:

1. $Z(p)$ and $Y(p) = 1/Z(p)$ of a passive LC two-terminal network are positive, and real in p .
2. Poles and zeros of $Z(p)$ and $Y(p)$ lie exclusively on the $j\omega$ -axis of the p -plane.
3. $Z(j\omega)$ and $Y(j\omega)$ are purely imaginary for all ω
4. All coefficients of the partial fraction representation of $Z(p)$ and $Y(p)$ are **positive and real** (without proof).



2.1.3 The passive RC two-terminal network function



2.1.3 The passive RC two-terminal network function

The passive RC two-terminal network contains no coils:

$$\longrightarrow T_z(p) = 0 \quad \forall \omega \quad \text{because } L_i = 0$$

Therefore the impedance function results to

$$Z(p) = F_Z(p) + \frac{1}{p}V_Z(p)$$

with

$$\operatorname{Re}\{Z(p)\} = F_Z(p) + \frac{\sigma}{\sigma^2 + \omega^2}V_Z(p)$$

$$\operatorname{Im}\{Z(p)\} = -\frac{\omega}{\sigma^2 + \omega^2}V_Z(p)$$



2.1.3 The passive RC two-terminal network function

If $p_0 = \sigma_0 + j\omega_0$ is a zero of $Z(p)$, then:

$$\operatorname{Re}\{Z(p_0)\} = F_Z(p_0) + \frac{\sigma_0}{\sigma_0^2 + \omega_0^2} V_Z(p_0) = 0$$

and
$$\operatorname{Im}\{Z(p_0)\} = -\frac{\omega_0}{\sigma_0^2 + \omega_0^2} V_Z(p_0) = 0$$

Discussion:

$$\operatorname{Im}\{Z(p_0)\} = 0 \Rightarrow V_Z(p_0) = 0 \text{ or } \omega_0 = 0$$

Property: $F_Z(p) \neq 0$ and $V_Z(p) \neq 0$ (due to RC network)

→
$$\operatorname{Im}\{Z(p_0)\} = 0 \text{ only in case of } \omega_0 = 0$$

So $\omega_0 = 0$ is a necessary condition for any zero!



2.1.3 The passive RC two-terminal network function

$$\rightarrow p_{0v} = \sigma_{0v} \quad \forall v$$

This means that all zeros can only lie on the real σ axis.

In this case for the real part of the impedance function holds:

$$\operatorname{Re} \{Z(\sigma_{0v})\} = F_Z(\sigma_{0v}) + \frac{1}{\sigma_{0v}} V_Z(\sigma_{0v}) = 0$$

This condition can only be satisfied for $\sigma_{0v} < 0$ which means that all zeros must lie in the left open p-plane!

In a similar manner it can be shown:

- All zeros of $Y(p)$ must lie in the left closed p- plane.
- These zeros lie on the real axis.



2.1.3 The passive RC two-terminal network function

Summary of the characteristics of the impedance function $Z(p)$:

1. $Z(p)$ or $Y(p) = 1/Z(p)$ are positive and real in p
2. The zeros of $Z(p)$ and thus the poles of $Y(p)$ exclusively lie in the left closed half p -plane and there on the real axis.
3. It can also be shown (without proof):
Poles and zeros of $Z(p)$ appear in alternating sequence on the real axis
4. $Z(p)$ can only have a single pole at $p = 0$, so $Y(p)$ can only have a single zero at $p = 0$.
5. The decomposition of $Z(p)$ or $Y(p)$ into partial fractions leads to positive real development coefficients (without proof).



2.1.3 The passive RC two-terminal network function

Partial fractions representation of such an impedance function $Z(p)$ look like:

$$Z(p) = \frac{A_0}{p} + \sum_{v=1}^N \frac{A_v}{p - \sigma_{\infty v}} + A_{\infty} \quad \text{with } \sigma_{\infty v} < 0; \quad A_0, A_v, A_{\infty} \text{ being positive real}$$

with:

$$A_0 = \lim_{p \rightarrow 0} \{p \cdot Z(p)\}$$

$$A_v = \lim_{p \rightarrow \sigma_{\infty v}} \{Z(p) \cdot (p - \sigma_{\infty v})\}$$

$$A_{\infty} = \lim_{p \rightarrow \infty} \{Z(p)\}$$



2.1.3 The passive RC two-terminal network function

Partial fractions representation of such an admittance function $Y(p)$ look like:

$$Y(p) = B_0 + \sum_{\mu=1}^M \frac{B_{\mu} \cdot p}{p - \sigma_{\infty\mu}} + B_{\infty} \cdot p$$

with $\sigma_{\infty\mu} < 0 \quad \forall \mu$ and B_0, B_{μ}, B_{∞} being positive real with:

$$B_0 = \lim_{p \rightarrow 0} Y(p)$$

$$B_{\infty} = \lim_{p \rightarrow \infty} \left\{ \frac{Y(p)}{p} \right\}$$

$$B_{\mu} = \lim_{p \rightarrow \sigma_{\infty\mu}} \left\{ \frac{Y(p)}{p} \cdot (p - \sigma_{\infty\mu}) \right\}$$



2.1.4 The passive RL two-terminal network function



2.1.4 The passive RL two-terminal network function

The passive RL two-terminal network contains no capacitors:

$$\longrightarrow V_z(p) = 0 \quad \forall \omega \quad \text{because } C_k = 0$$

Therefore the impedance function results to

$$Z(p) = F_z(p) + p \cdot T_z(p)$$

with

$$\operatorname{Re}\{Z(p)\} = F_z(p) + \sigma \cdot T_z(p)$$

$$\operatorname{Im}\{Z(p)\} = \omega \cdot T_z(p)$$



2.1.4 The passive RL two-terminal network function

If $p_0 = \sigma_0 + j\omega_0$ is a zero of $Z(p)$, then the following must be true:

$$\operatorname{Re}\{Z(p_0)\} = F_Z(p_0) + \sigma_0 \cdot T_Z(p_0) = 0$$

and $\operatorname{Im}\{Z(p_0)\} = \omega_0 \cdot T_Z(p_0) = 0$

Discussion:

Similar to the case of the RC two-terminal networks it follows:

$$\operatorname{Im}\{Z(p_0)\} = 0 \quad \text{only in case of} \quad \omega_0 = 0$$

→ $p_{0v} = \sigma_{0v} \quad \text{with} \quad \sigma_{0v} < 0 .$

Additional considerations conc. $Y(p)$ lead in total to the next statements:



2.1.4 The passive RL two-terminal network function

Summary:

1. $Z(p)$ and $Y(p)$ are positive, real and rational in p
2. The pole and zeros of $Z(p)$ and $Y(p)$ only lie in the left closed p -half plane
3. They only lie on the real axis
4. There are only single poles and zeros
5. The coefficients in the partial fraction expansion are positive



2.1.4 The passive RL two-terminal network function

Partial fraction representation of such an impedance function $Z(p)$:

$$Z(p) = A_0 + \sum_{v=1}^N \frac{p \cdot A_v}{p - \sigma_{\infty v}} + p \cdot A_{\infty}$$

with $\sigma_{\infty v} < 0$ and A_0, A_v, A_{∞} being positive real with:

$$A_0 = \lim_{p \rightarrow 0} \{Z(p)\}$$

$$A_v = \lim_{p \rightarrow \sigma_{\infty v}} \left\{ \frac{Z(p)}{p} \cdot (p - \sigma_{\infty v}) \right\}$$

$$A_{\infty} = \lim_{p \rightarrow \infty} \left\{ \frac{Z(p)}{p} \right\}$$



2.1.4 The passive RL two-terminal network function

Partial fraction representation of a corresponding admittance function $Y(p)$:

$$Y(p) = \frac{B_0}{p} + \sum_{\mu=1}^M \frac{B_{\mu}}{p - \sigma_{\infty\mu}} + B_{\infty}$$

with $\sigma_{\infty\mu} < 0 \quad \forall \mu$ and B_0, B_{μ}, B_{∞} being positive real with

$$B_0 = \lim_{p \rightarrow 0} \{p \cdot Y(p)\}$$

$$B_{\mu} = \lim_{p \rightarrow \sigma_{\infty\mu}} \{Y(p) \cdot (p - \sigma_{\infty\mu})\}$$

$$B_{\infty} = \lim_{p \rightarrow \infty} \{Y(p)\}$$



Chapter 2

Characteristics and realization of passive two-terminal network function

2.2 Design of a passive two-terminal network



2.2.1 Realization of a LC passive two-terminal network

From the partial fraction representation of the impedance function

$$Z(p) = \frac{A_0}{p} + \sum_{v=1}^N \frac{2 \cdot A_v \cdot p}{p^2 + \omega_{\infty v}^2} + A_{\infty} \cdot p \quad \text{with } A_0, A_v, A_{\infty} \text{ being real and positive}$$

of a lossless two-terminal network one can derive:

↳ Each individual addend corresponds to a single impedance connected in series.

The first addend gives:

$$Z_0(p) = \frac{A_0}{p} = \frac{1}{\frac{1}{A_0} \cdot p} \quad \xrightarrow{\text{Impedance of a capacitor}} \quad C_0 = \frac{1}{A_0}$$



2.2.1 Realization of a LC passive two-terminal network

The further addends of the fractions give:

$$Z_v(p) = \frac{2 \cdot A_v \cdot p}{p^2 + \omega_{\infty v}^2} = \frac{1}{\frac{1}{2 \cdot A_v} \cdot p + \frac{\omega_{\infty v}^2}{2 \cdot A_v} \cdot \frac{1}{p}}$$

They correspond in each case to the parallel connection of

- a capacitor
- and
- a coil

$$C_v = \frac{1}{2 \cdot A_v}$$

$$L_v = \frac{2 \cdot A_v}{\omega_{\infty v}^2}$$



2.2.1 Realization of a LC passive two-terminal network

The last addend corresponds to the impedance of a coil:

$$L_{\infty} = A_{\infty}$$

This leads directly to the 1st FOSTER form (canonical circuit):

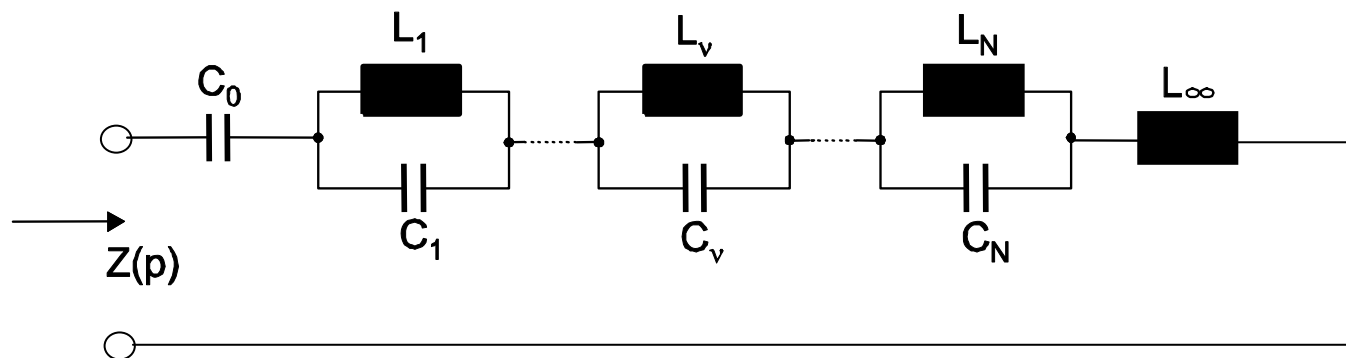


Fig.: Realization of the LC two-terminal impedance $Z(p)$ as partial fraction circuit

2.2.1 Realization of a LC passive two-terminal network

From the partial fraction representation of the admittance function

$$Y(p) = \frac{B_0}{p} + \sum_{\mu=1}^M \frac{2 \cdot B_{\mu} \cdot p}{p^2 + \omega_{\infty\mu}^2} + B_{\infty} \cdot p \quad \text{with } B_0, B_{\mu}, B_{\infty} \text{ being real and positive}$$

one can derive:

↳ Each individual addend of the partial fractions represents a single admittance which is connected in parallel to the others.

The first addend gives:

$$\frac{B_0}{p} = \frac{1}{\frac{1}{B_0} \cdot p} \quad \xrightarrow{\text{Admittance of an inductance}} \quad L_0 = \frac{1}{B_0}$$



2.2.1 Realization of a LC passive two-terminal network

The further addends of the form:

$$Y_{\mu}(p) = \frac{2 \cdot B_{\mu} \cdot p}{p^2 + \omega_{\infty\nu}^2} = \frac{1}{\frac{1}{2 \cdot B_{\mu}} \cdot p + \frac{\omega_{\infty\nu}^2}{2 \cdot B_{\mu}} \cdot \frac{1}{p}}$$

correspond in each case to the **serial connection of**

• a coil:

and

• a capacitor:

$$L_{\mu} = \frac{1}{2 \cdot B_{\mu}}$$

$$C_{\mu} = \frac{2 \cdot B_{\mu}}{\omega_{\infty\mu}^2}$$



2.2.1 Realization of a LC passive two-terminal network

The last addend corresponds to the admittance of a capacitor:

$$C_{\infty} = B_{\infty}$$

Thus the 2nd FOSTER form is obtained (canonical circuit):

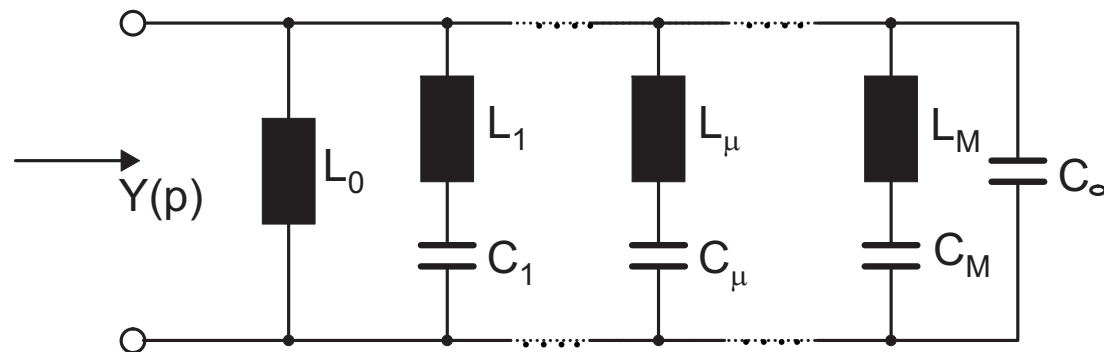


Fig.: Realization of the LC two-terminal admittance $Y(p)$ as a partial fraction circuit

2.2.1 Realization of a LC passive two-terminal network

The first CAUER form procedure is a method to set up two-terminal networks from a continued fraction:

Step 1: Pick up from $Z(p)$ the last addend $A_\infty \cdot p$, so that the remainder is:

$$Z_1(p) = Z(p) - A_\infty \cdot p$$

Step 2: The remainder admittance will then be: $\longrightarrow Y_1(p) = \frac{1}{Z_1(p)}$

Step 3: Take off from the remainder admittance $Y_1(p)$ the term $B_{\infty 1} \cdot p$, so that:

$$Y_2(p) = Y_1(p) - B_{\infty 1} \cdot p$$

Step 4: Inverting $Y_2(p)$ gives the impedance of single LC two-pole network:

$$Z_2(p) = \frac{1}{Y_2(p)}$$



2.2.1 Realization of a LC passive two-terminal network

A continued application leads to a fraction representation of the first CAUER form:

$$Z(p) = A_{\infty} \cdot p + \frac{1}{B_{\infty 1} \cdot p + \frac{1}{A_{\infty 2} \cdot p + \frac{1}{B_{\infty 3} \cdot p + \frac{1}{A_{\infty 4} \cdot p + \dots}}}}$$


The procedure ends if none of the following $A_{\infty \nu} \cdot p$ or $B_{\infty \mu} \cdot p$ expressions remains:

Note: Both are poles located at p going to infinite!



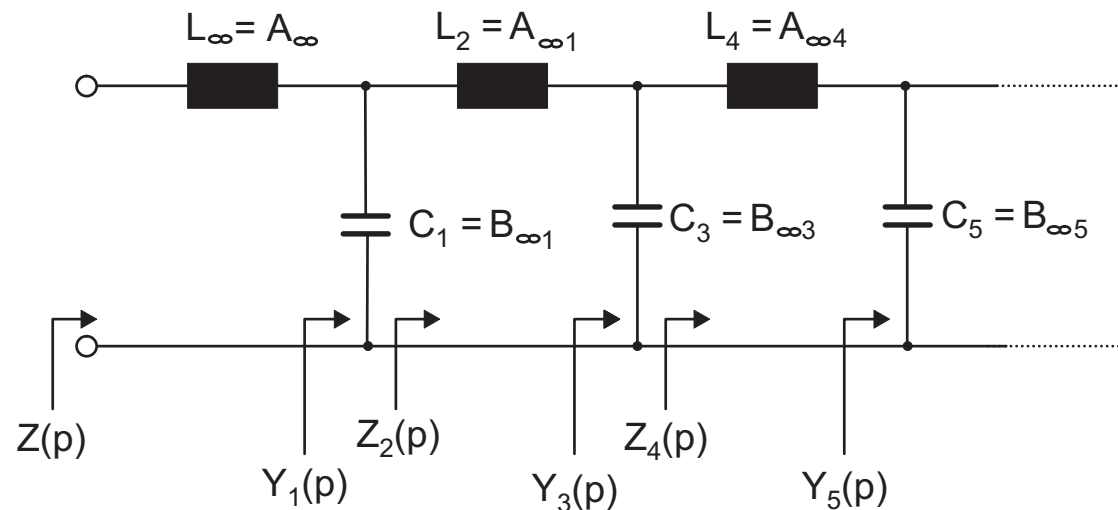2.2.1 Realization of a LC passive two-terminal network

The appropriate continued fraction - or also branch circuit looks as follows:



Realization of the LC two-terminal impedance as a continued fraction circuit (First CAUER form)

In the realized circuit, inductances are in the long branches and capacitors are in the transverse branches.

2.2.1 Realization of a LC passive two-terminal network

Background of the method

- $Z_1(p) = Z(p) - A_{\infty}p$ exhibits a zero for $p \rightarrow \infty$ due to C_1
- Thus $Y_1(p) = 1/Z_1(p)$ has a pole for $p \rightarrow \infty$
and a development coefficient $B_{\infty 1}$
- $Y_2(p) = Y_1(p) - B_{\infty 1}p$ has a zero at $p \rightarrow \infty$ due to L_2
- Thus $Z_2(p) = 1/Y_2(p)$ has a pole for $p \rightarrow \infty$
and a development coefficient $A_{\infty 2}$
- $Z_3(p) = Z_2(p) - A_{\infty 2}p$ has a zero at $p \rightarrow \infty$ due to C_3
... and so on.

So this method always takes off the pole at infinitely large p !



2.2.1 Realization of a LC passive two-terminal network

Other comments

- It is also possible to write an admittance function $Y(p)$ as a continued fraction
- Such a procedure in general follows the 4 steps given above
- The difference is: The procedure starts with step 3!
- Thus the circuits show the same structure as in the previous figure
- The difference here: Coils and capacitors are exchanged



2.2.1 Realization of a LC passive two-terminal network

Second CAUER form procedure (with taking off poles at $p = 0$):

Step 1: From the given $Z(p)$, the term A_0 / p is taken off, thus the remainder is:

$$Z_1(p) = Z(p) - \frac{A_0}{p}$$

Step 2: The corresponding admittance is formed by: $\longrightarrow Y_1(p) = \frac{1}{Z_1(p)}$

Step 3: The term B_{01} / p is taken off from the remainder of $Y_1(p)$:

$$Y_2(p) = Y_1(p) - \frac{B_{01}}{p}$$

Step 4: The impedance is the defined by the inverse of the remainder:

$$Z_2(p) = \frac{1}{Y_2(p)}$$



2.2.1 Realization of a LC passive two-terminal network

Thus one obtains the following LC-impedance function $Z(p)$:


$$Z(p) = \frac{A_0}{p} + \frac{1}{\frac{B_{01}}{p} + \frac{1}{\frac{A_{02}}{p} + \frac{1}{\frac{B_{03}}{p} + \frac{1}{\frac{A_{04}}{p} + \dots}}}}}$$

→ The procedure described above ends as soon as no more expressions can be taken off!



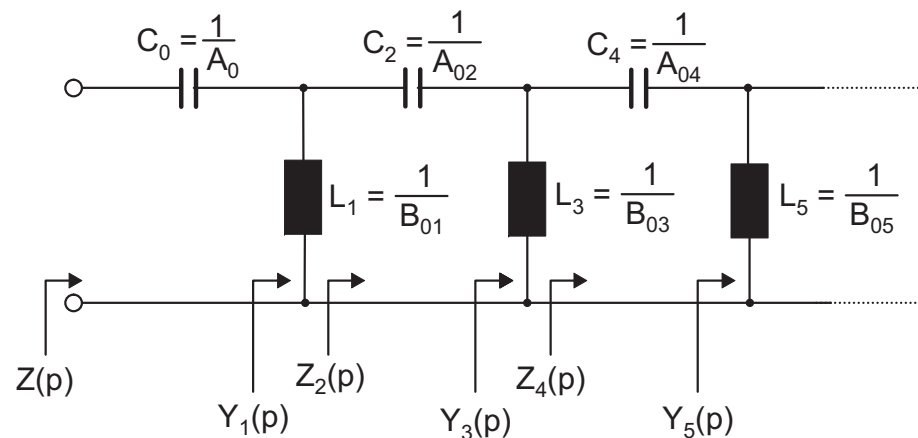2.2.1 Realization of a LC passive two-terminal network

The appropriate continued fraction or branch circuit then looks as follows:



Realization of the LC two-terminal impedance $Z(p)$ in the 2nd CAUER form



One obtains a network which contains capacitors in the long branches and inductances in the transverse branches.

2.2.2 Realization of a RC passive two-terminal network

Based on the partial fraction representation of the impedance function

$$Z(p) = \frac{A_0}{p} + \sum_{v=1}^N \frac{A_v}{p - \sigma_{\infty v}} + A_{\infty} \text{ with } \sigma_{\infty v} < 0; \quad A_0, A_v, A_{\infty} : \text{positive real}$$

one can interpret it as follows:

The last addend A_{∞} of the summation

$R_{\infty} = A_{\infty} \longrightarrow$ is the impedance of a **resistance**



2.2.2 Realization of a RC passive two-terminal network

The further addends of the form

$$Z_\nu(p) = \frac{A_\nu}{p - \sigma_{\infty\nu}} = \frac{1}{\frac{1}{A_\nu} \cdot p + \frac{|\sigma_{\infty\nu}|}{A_\nu}} \text{ due to } \sigma_{\infty\nu} < 0 \forall \nu$$

correspond in each case to the **parallel connection** of

• a capacitor

and

• a resistor

$$C_\nu = \frac{1}{A_\nu}$$

$$R_\nu = \frac{A_\nu}{|\sigma_{\infty\nu}|}$$




2.2.2 Realization of a RC passive two-terminal network

The first addend of the summation is A_0/p .

This corresponds to the impedance of the capacity: $C_0 = \frac{1}{A_0}$

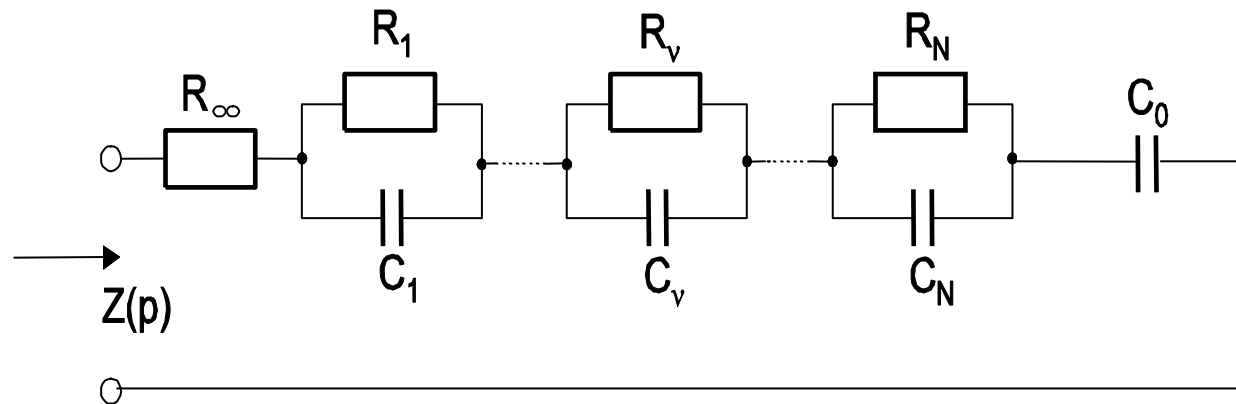Thus it results the partial fraction circuit or **1st FOSTER form** of an RC circuit:



Realization of the RC two-terminal partial fraction circuit

2.2.2 Realization of a RC passive two-terminal network

In case of the partial fractions representation of the admittance function one obtains:

$$Y(p) = B_0 + \sum_{\mu=1}^M \frac{B_{\mu} \cdot p}{p - \sigma_{\infty\mu}} + B_{\infty} \cdot p$$

with $\sigma_{\infty\mu} < 0$ and B_0, B_{μ}, B_{∞} being positive real

This means that **the first addend**

$$R_0 = \frac{1}{B_0} \longrightarrow \text{corresponds to a resistor}$$



2.2.2 Realization of a RC passive two-terminal network

The further addends of the form

$$Y_{\mu}(p) = \frac{B_{\mu}p}{p - \sigma_{\infty\mu}} = \frac{1}{\frac{1}{B_{\mu}} + \frac{|\sigma_{\infty\mu}|}{B_{\mu}} \cdot \frac{1}{p}} \quad \text{due to } \sigma_{\infty\mu} < 0 \quad \forall \mu$$

correspond in each case to the **series connection** of:

- a resistor
- and
- a capacitor

$$R_{\mu} = \frac{1}{B_{\mu}}$$

$$C_{\mu} = \frac{B_{\mu}}{|\sigma_{\infty\mu}|}$$




2.2.2 Realization of a RC passive two-terminal network

The last addend $B_\infty \cdot p$ corresponds to the admittance of a capacitor:

$$C_\infty = B_\infty$$

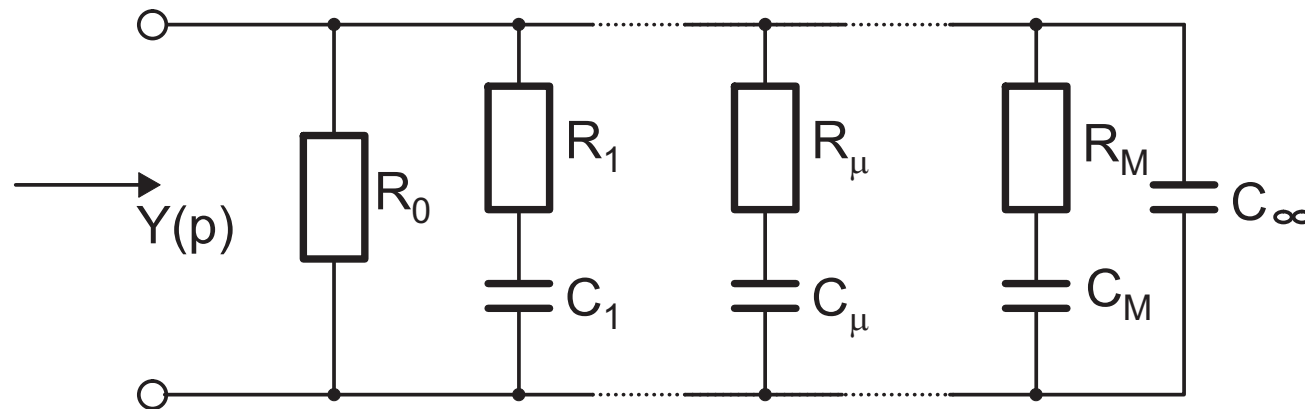Thus the corresponding partial fractions circuit looks as follows:



Realization of the RC two-terminal admittance $Y(p)$ as partial fraction circuit
(Second FOSTER form)

2.2.2 Realization of a RC passive two-terminal network

Just as LC two-terminal networks, the impedance function $Z(p)$ and the admittance function $Y(p)$ of a passive RC network can also be written as a continued fraction with a corresponding (branch) circuit, either by:

- The 4-step method of first CAUER form by taking off poles with $p = \infty$ in which:

→ Resistors are in the long branches and the capacitors are in the transverse branches of the branch circuit or

- The 4-step method of second CAUER form by taking off poles with $p = 0$ in which:

→ Capacitors are in the long branches and resistors are in the transverse branches of the branch circuit



2.2.2 Realization of a RC passive two-terminal network


The assigned continued fraction representation (First CAUER Form):

$$Z(p) = A_{\infty} + \frac{1}{B_{\infty 1} \cdot p + \frac{1}{A_{\infty 2} + \frac{1}{B_{\infty 3} \cdot p + \frac{1}{A_{\infty 4} \cdot \dots}}}}$$



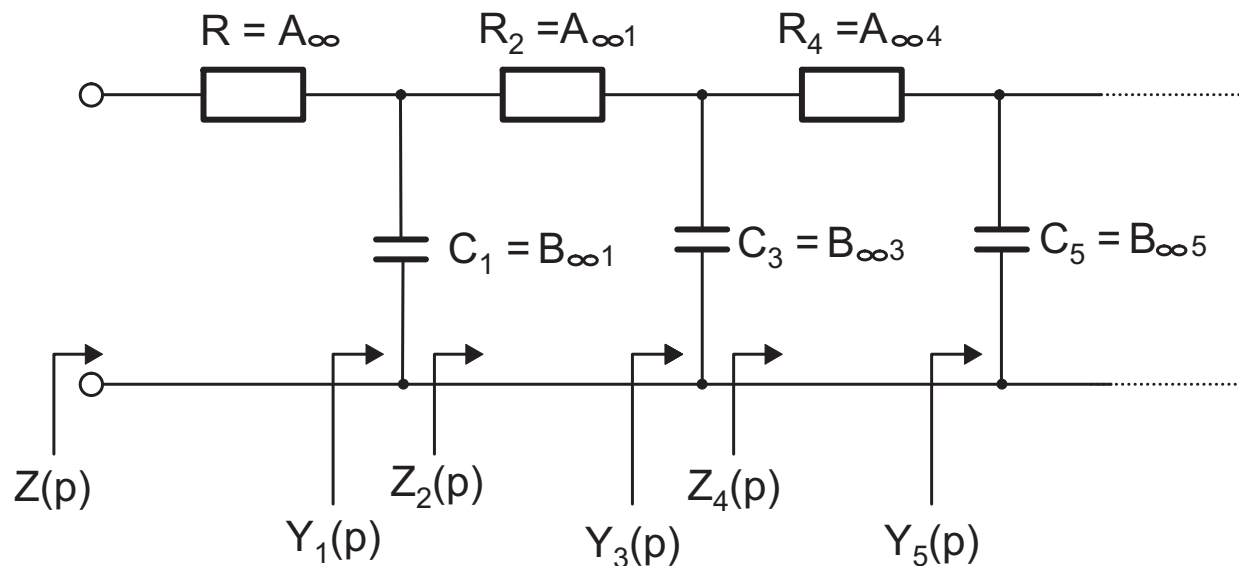2.2.2 Realization of a RC passive two-terminal network

The appropriate continued fraction or branch circuit looks as follows:



Realization of the RC two-terminal network $Z(p)$ as continued fraction branch circuit (1st CAUER form)

2.2.2 Realization of a RC passive two-terminal network


The assigned continued fraction representation (Second CAUER form):

$$Z(p) = \frac{A_0}{p} + \frac{1}{B_{01} + \frac{1}{\frac{A_{02}}{p} + \frac{1}{B_{03} + \frac{1}{\frac{A_{04}}{p} + \dots}}}}$$



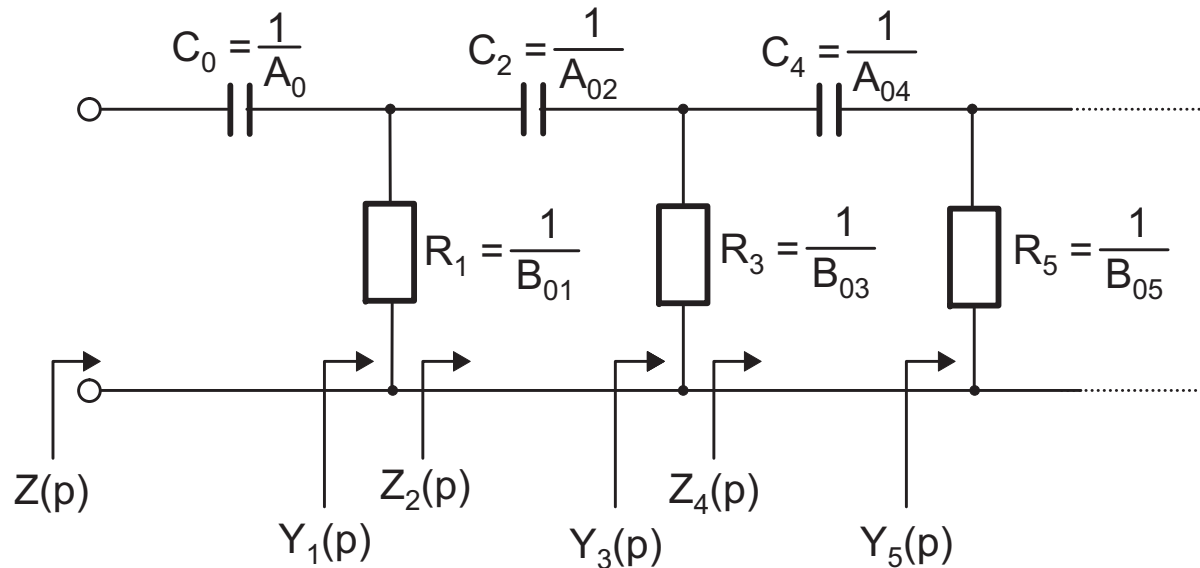2.2.2 Realization of a RC passive two-terminal network

The appropriate continued fraction or branch circuit:



Realization of the RC two-terminal network $Z(p)$ as continued fraction
Branch circuit (Second CAUER form)

2.2.3 Realization of a RL passive two-terminal network

The partial fractions representation of the impedance function $Z(p)$ gives:

$$Z(p) = A_0 + \sum_{v=1}^N \frac{p \cdot A_v}{p + \sigma_{\infty v}} + p \cdot A_{\infty} \quad \text{with } \sigma_{\infty v} < 0; \quad A_0, A_v, A_{\infty} \text{ are positive real}$$

One can interpret again each individual addend as a single impedance and translate the sum of partial fractions into a serial connection of single impedances.

The first addend is considered as:

$$R_0 = A_0 \longrightarrow \text{impedance of a resistance}$$



2.2.3 Realization of a RL passive two-terminal network

The further addends of the form

$$Z_v(p) = \frac{A_v \cdot p}{p - \sigma_{\infty v}} = \frac{1}{\frac{1}{A_v} + \frac{|\sigma_{\infty v}|}{A_v} \cdot \frac{1}{p}}$$

correspond in each case to the **parallel connection** of

• a resistor and

$$R_v = A_v$$

• a coil

$$L_v = \frac{A_v}{|\sigma_{\infty v}|}$$




2.2.3 Realization of a RL passive two-terminal network

The last addend $A_{\infty}p$ corresponds to the impedance of a coil:

$$L_{\infty} = A_{\infty}$$

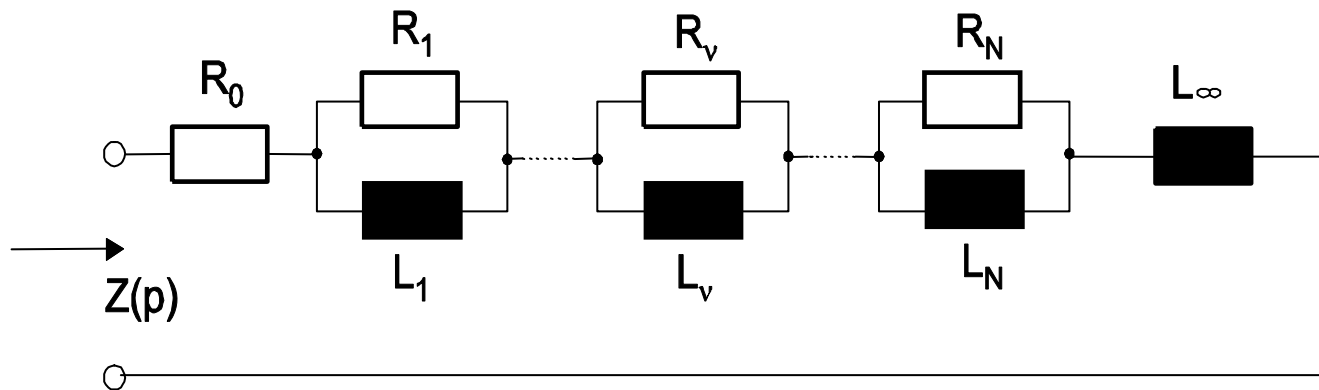Then the assigned partial fractions circuit of $Z(p)$ - (in first FOSTER form) results:



Realization of the RC two-terminal impedance function $Z(p)$ as partial fractions circuit (First FOSTER form)

2.2.3 Realization of a RL passive two-terminal network

The partial fraction representation of the admittance function $Y(p)$ has the form:

$$Y(p) = \frac{B_0}{p} + \sum_{\mu=1}^M \frac{B_{\mu}}{p - \sigma_{\infty\mu}} + B_{\infty}$$

with $\sigma_{\infty\mu} < 0$ and B_0, B_{μ}, B_{∞} being positive real

The last term arising in the sum

→ corresponds to the admittance of a resistor:

$$R_{\infty} = \frac{1}{B_{\infty}}$$



2.2.3 Realization of a RL passive two-terminal network

The further adds

$$Y_{\mu}(p) = \frac{B_{\mu}}{p - \sigma_{\infty\mu}} = \frac{1}{\frac{p}{B_{\mu}} + \frac{|\sigma_{\infty\mu}|}{B_{\mu}}}$$

become in each case a series connection of

- a coil: $L_{\mu} = \frac{1}{B_{\mu}}$

- and a resistor $R_{\mu} = \frac{|\sigma_{\infty\mu}|}{B_{\mu}}$




2.2.3 Realization of a RL passive two-terminal network

The first term of the form

$$L_0 = \frac{1}{B_0} \longrightarrow \text{corresponds to the admittance of a coil.}$$

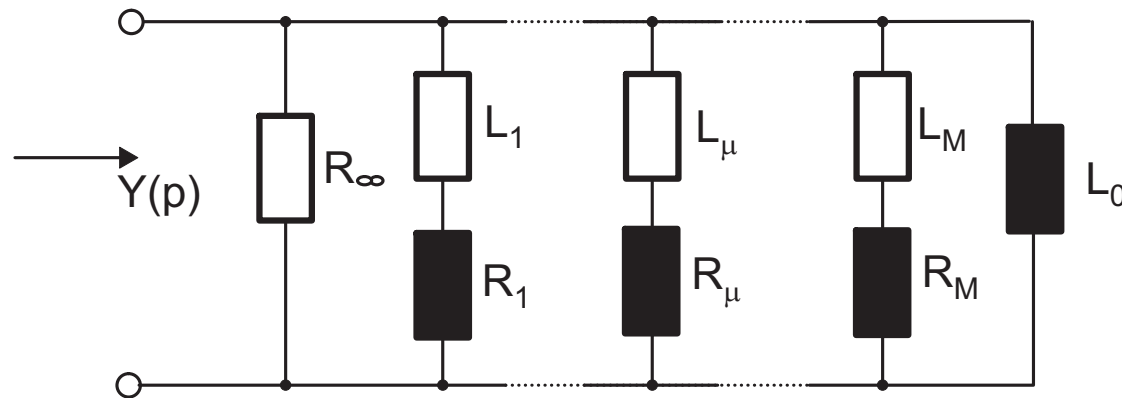The resulting partial fraction circuit looks as follows:



Realization of the RL two-terminal admittance function $Y(p)$ as partial fractions circuit (Second FOSTER form)

Summary – Partial fractions method

For LC networks:

$$Z(p) = \frac{A_0}{p} + \sum_{v=1}^N \frac{2 \cdot A_v \cdot p}{p^2 + \omega_{\infty v}^2} + A_{\infty} \cdot p \quad \text{with } A_0, A_v, A_{\infty} : \text{real and positive}$$

$$Y(p) = \frac{B_0}{p} + \sum_{\mu=1}^M \frac{2 \cdot B_{\mu} \cdot p}{p^2 + \omega_{\infty \mu}^2} + B_{\infty} \cdot p \quad \text{with } B_0, B_{\mu}, B_{\infty} \text{ being real and positive}$$

For RC networks:

$$Z(p) = \frac{A_0}{p} + \sum_{v=1}^N \frac{A_v}{p - \sigma_{\infty v}} + A_{\infty} \quad \text{with } \sigma_{\infty v} < 0$$

$$Y(p) = B_0 + \sum_{\mu=1}^M \frac{B_{\mu} \cdot p}{p - \sigma_{\infty \mu}} + B_{\infty} \cdot p \quad \text{with } \sigma_{\infty \mu} < 0 \text{ and } B_0, B_{\mu}, B_{\infty} \text{ being positive real}$$

For RL networks:

$$Z(p) = A_0 + \sum_{v=1}^N \frac{p \cdot A_v}{p - \sigma_{\infty v}} + p \cdot A_{\infty} \quad \text{with } \sigma_{\infty v} < 0$$

$$Y(p) = \frac{B_0}{p} + \sum_{\mu=1}^M \frac{B_{\mu}}{p - \sigma_{\infty \mu}} + B_{\infty} \quad \text{with } \sigma_{\infty \mu} < 0$$



Summary – Chain of fractions method

$$\text{LC networks: } Z(p) = \frac{A_0}{p} + \frac{1}{\frac{B_{01}}{p} + \frac{1}{\frac{A_{02}}{p} + \frac{1}{\frac{B_{03}}{p} + \frac{1}{\frac{A_{04}}{p} + \dots}}}}}$$

$$\text{RC networks: } Z(p) = \frac{A_0}{p} + \frac{1}{B_{01} + \frac{1}{\frac{A_{02}}{p} + \frac{1}{B_{03} + \frac{1}{\frac{A_{04}}{p} + \dots}}}}}$$

