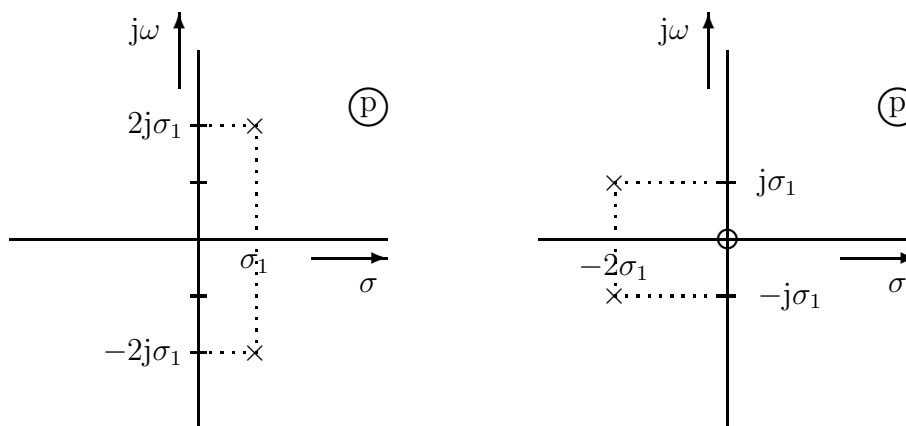


Chapter 1 – Introduction and Basics

**Problem 1.1**

The following two pole-zero-plots describe the system functions of the two-ports A and B, whereby the value  $\sigma_1 > 0$ .



- 1.1.1 Determine the system functions  $H_{LA}(p)$  and  $H_{LB}(p)$  of both two-ports.
- 1.1.2 Determine the transfer functions  $H_A(\omega) = H_{LA}(p = j\omega)$  and  $H_B(\omega) = H_{LB}(p = j\omega)$  of both two-ports.
- 1.1.3 Which kind of systems are described by the two-ports A and B. Justify your answer.
- 1.1.4 Determine the impulse response  $h_A(t)$  and  $h_B(t)$  of the system functions  $H_{LA}(p)$  and  $H_{LB}(p)$ .
- 1.1.5 Give a short comment on the stability of both two-ports.

**Problem 1.2**


The following system function  $H_L(p)$  of a linear, time invariant two-port is given:

$$H_L(p) = \frac{U_2(p)}{U_1(p)} = \frac{p}{p^2 + 2ap + b} \quad \text{with } a, b \text{ real and positive}$$

- 1.2.1 Determine the poles and zeros and name the conditions for  $H_L(p)$  being a system function of a stable two-port.
- 1.2.2 Calculate the impulse response  $h(t)$ , which is the back-transformed system function  $H_L(p)$ , for  $a = 3$  and  $b = 8$ .
- 1.2.3 Which kind of system is described by the two-port?

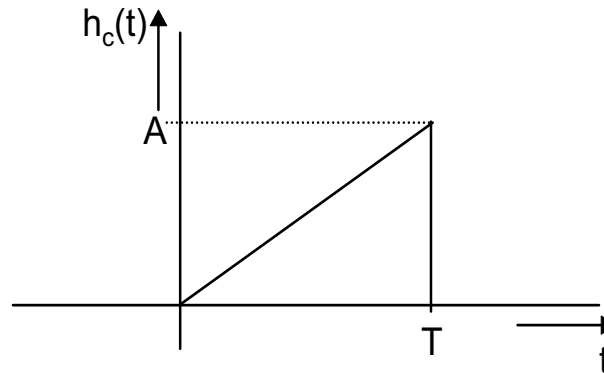**Problem 1.3**

The following impulse response  $h_c(t)$  should be approximated using a linear, time invariant two-port.



- 1.3.1 Describe  $h_c(t)$  as a sum of weighted and time-shifted ramp- and step-functions.
- 1.3.2 Determine the Laplace-Transformed  $H_{Lc}(p)$  of  $h_c(t)$  using the result of 1.3.1.
- 1.3.3 Using  $H_{Lc}(p)$  develop an approximated function  $H_{La}(p)$  by substituting the term  $e^{pT}$  by  $e^{pT} = 1 + pT + (pT)^2/2 + \dots$ , truncating after the third term of the series expansion.
- 1.3.4 Draw the pole-zero-plot of  $H_{La}(p)$ .
- 1.3.5 Determine  $h_a(t)$ , which is the Laplace-back-transformed of  $H_{La}(p)$  and sketch  $h_a(t)$ .


**Problem 1.4**

Given is a graph with  $n$  nodes, in which each node is connected to all other nodes by a branch.

- 1.4.1 Draw the graphs for  $n = 2(1)5$ .
- 1.4.2 Derive a formula for the calculation of the number  $z(n)$  of branches of each graph.
- 1.4.3 Draw for  $n = 2(1)5$  all complete trees of each graph.
- 1.4.4 Derive the formula for the calculation of the number  $z_u(n)$  of independent branches of a graph.

**Problem 1.5**

The following network is given:

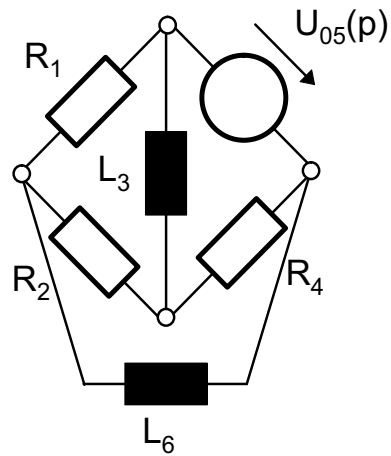

- 1.5.1 Outline a complete tree.
- 1.5.2 Determine the incidence matrix  $\vec{M}$  of the previously outlined tree.
- 1.5.3 Determine the branch impedance matrix  $\vec{Z}_{BI}$ .
- 1.5.4 Determine the loop impedance matrix  $\vec{Z}$ .

**Problem 1.6**

Given is the following incidence matrix:

$$\vec{M} = \begin{pmatrix} 1 & 0 & 0 \\ 1 & -1 & 0 \\ 0 & 1 & 0 \\ 0 & 1 & -1 \\ 0 & 0 & 1 \end{pmatrix}$$

which connects the branch current vector  $\vec{I}$  with the loop current vector  $\vec{J}$  according to  $\vec{I} = \vec{M} \cdot \vec{J}$ . Further on the branch impedance matrix


$$\vec{Z}_{\text{BI}} = \begin{pmatrix} 1/pC_1 & 0 & 0 & 0 & 0 \\ 0 & 0 & 0 & 0 & 0 \\ 0 & 0 & pL_3 & 0 & 0 \\ 0 & 0 & 0 & R_4 & 0 \\ 0 & 0 & 0 & 0 & 1/pC_5 \end{pmatrix}$$

of the network is given. This network is powered by an independent voltage source with the voltage  $U_{s\nu}(p)$ .

- 1.6.1 Determine the number  $k$  of nodes.
- 1.6.2 Denote the loop currents  $\vec{J}_\mu(p)$  and the independent branches of the network by specifying the indices  $\mu$ .
- 1.6.3 Determine the loop impedance matrix  $\vec{Z}$  of the network.
- 1.6.4 Determine the voltage source vector  $\vec{U}_s(p)$ .
- 1.6.5 Draw the corresponding directed graph of the network, insert the branch indices  $\nu$  and indicate the complete tree of the graph by drawing the corresponding branches with thick lines.
- 1.6.6 Draw the network using the symbols of the network elements and denote those elements.
- 1.6.7 Determine the components  $J_\mu(p)$  of the loop current vector  $\vec{J}(p)$ .
- 1.6.8 Determine the components  $I_\nu(p)$  of the branch current vector  $\vec{I}(p)$ .
- 1.6.9 Determine the components  $U_\nu(p)$  of the branch voltage vector  $\vec{U}(p)$ .

**Problem 1.7**


The following network is given.

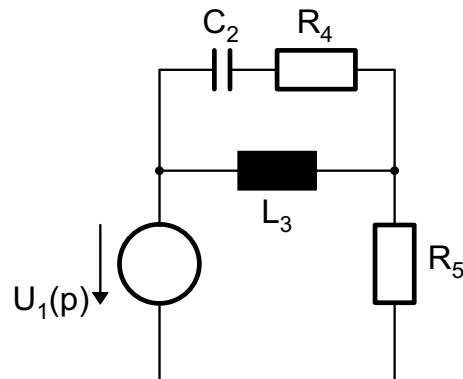

- 1.7.1 Draw a directed graph of the network and underline the branches of one complete tree. Denote each branch and the loop currents  $J_\mu(p)$ .
- 1.7.2 Calculate the number  $z_u$  of independent branches.
- 1.7.3 Determine the incidence matrix  $\vec{M}$ , which links the loop current vector  $\vec{J}$  and the branch current vector  $\vec{I}$  according to  $\vec{I}(p) = \vec{M} \cdot \vec{J}(p)$
- 1.7.4 Determine the branch impedance matrix  $\vec{Z}_{\text{Bl}}$ , the loop impedance matrix  $\vec{Z}$  and the branch voltage vector  $\vec{U}(p)$  of the network.

**Problem 1.8**

The following network is given.

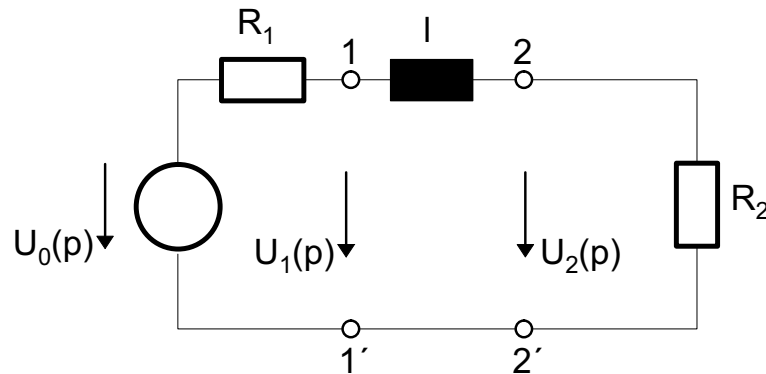

- 1.8.1 Determine the cascade matrix  $\vec{A}$  of the two-port, which is given by the nodes 1 and 1' at the input and 2 and 2' at the output.
- 1.8.2 Determine the 'operational effective function'  $H_{LB}(p)$ .
- 1.8.3 Plot the pole-zero-diagram of  $H_{LB}(p)$ .
- 1.8.4 Determine the normalised function  $H_{LBn}(\rho)$  with


$$\rho = \frac{p}{\omega_n} = \frac{\sigma}{\omega_n} + j\frac{\omega}{\omega_n} = \varsigma + j\Omega$$

using the normalised angular frequency  $\omega_n$ , which is the  $-3$  dB-cut-off-frequency of  $|H_{LB}(j\omega)|$ . Further on use the normalising resistance  $R_N$  which corresponds to the resistance  $R_1$ .


- 1.8.5 Determine the normalised transfer function  $H_{Fn}(\Omega) = H_{LBn}(j\Omega)$ .

**Problem 1.9**

Given is the following network

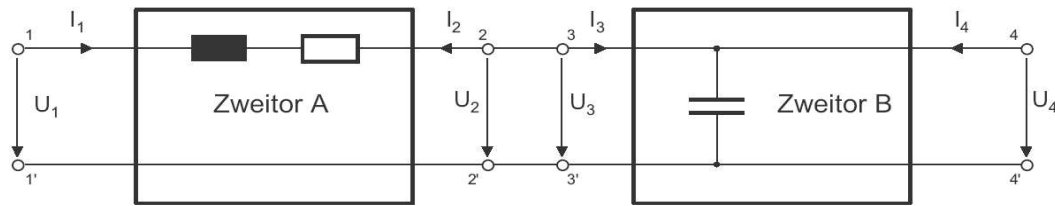


and its equivalent circuit diagram

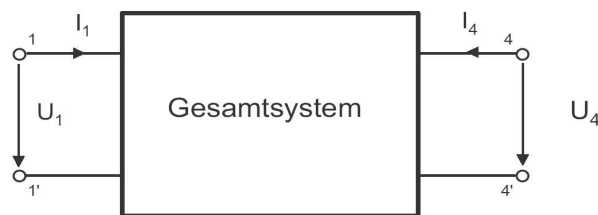

- 1.9.1 Determine the cascade matrices  $\overleftrightarrow{A}_a$  and  $\overleftrightarrow{A}_b$  of both two-ports, which are given by the nodes 1, 1', 2, 2', 3, 3', 4 and 4'.
- 1.9.2 Determine the cascade matrix  $\overleftrightarrow{A}_{ges}$  of the equivalent circuit diagram, where  $\overleftrightarrow{A}_a$  and  $\overleftrightarrow{A}_b$  are cascaded.

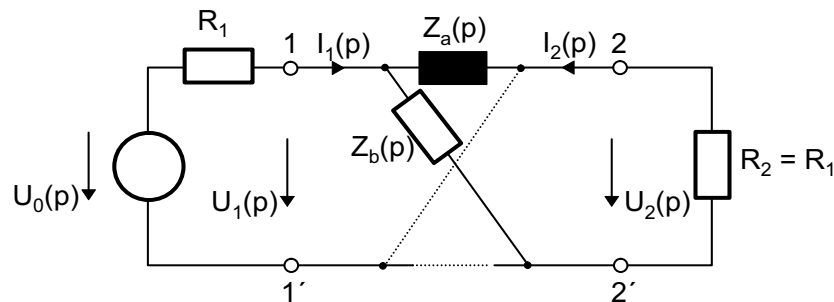**Problem 1.10**

Given is the following symmetric bridge two-port



Between the impedances  $Z_a(p)$  and  $Z_b(p)$  the relation  $Z_a \cdot Z_b = R_1^2$  is assumed.

- 1.10.1 Determine the impedance matrix  $\vec{Z}$  of the two-port.
- 1.10.2 Determine the 'operational effective function'  $H_{LB}(p)$  of the network.
- 1.10.3 Determine  $Z_a(p)$  and  $Z_b(p)$  as functions of  $R_1$  and  $H_{LB}(p)$ .
- 1.10.4 Which condition  $|H_{LB}(p = j\omega)|$  has to fulfill in order to be realised by passive RLC-elements?


Note 1: Which values  $\Re\{Z_a(p)\}$  and  $\Re\{Z_b(p)\}$  can assume?

Note 2: Substitute  $H_{LB} = H_r(p) + jH_i(p)$ .



**Problem 1.11**

Given is a symmetric bridge two-port

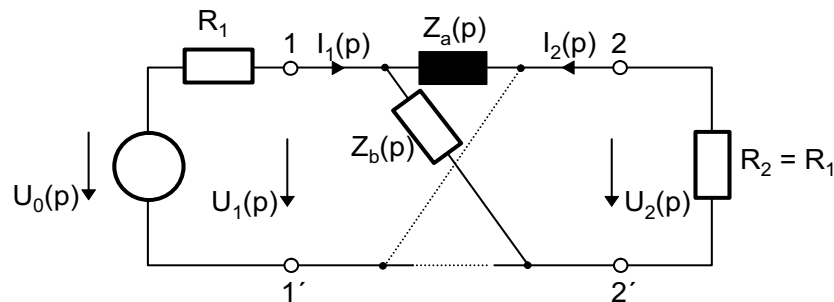

Further on  $Z_a(p) = pL$  and the 'operational effective function'  $H_{LB}(p)$  is given as:

$$H_{LB}(p) = \frac{k}{(p - p_\infty)(p - p_\infty^*)}$$

with  $p_\infty = -2\omega_0 + j\omega_0$ ,  $\omega_0 > 0$  and  $k$  real and positive.

- 1.11.1 Sketch the pole-zero-plot of  $H_{LB}(p)$  and determine the unit of  $k$ .
- 1.11.2 Which type of filter is described by the given  $H_{LB}(p)$ ? Why?
- 1.11.3 Which condition  $k$  has to fulfill if the given 'operational effective function'  $H_{LB}(p)$  has to be realised by passive RLC components?
- 1.11.4 Determine  $Z_b(p)$  using the result of 1.11.3

**Problem 1.12**

Given is a linear time invariant system with the impulse response

$$h(t) = \frac{1}{T_0} \text{rect}\left(\frac{t-T}{T}\right)$$


- 1.12.1 Sketch the impulse response  $h(t)$  as a function of the time  $t$  and chart important abscissa and ordinate values.
- 1.12.2 Determine the system function  $H_L(p) = \mathcal{L}\{h(t)\}$ .
- 1.12.3 Determine the poles and zeros of  $H_L(p)$  and sketch them in a pole-zero-plot.
- 1.12.4 Determine the normalised impulse response  $h_n(\tau)$  for the normalised time  $T_N = 1$  ms. Further on  $T_0 = 1$  ms and  $T = 2$  ms. Sketch  $h_n(\tau)$  as function of  $\tau$ .
- 1.12.5 Determine the normalised Laplace-transformed  $S_{nL}(\rho)$  for the normalised frequency  $\omega_N = 1/T_N$ .

**Problem 1.13**

As a first result for the realisation of a network function, the two-port A has been calculated. This two-port is constituted by three not coupled inductances  $L_1$ ,  $L_2$  and  $L_3$ . The negative inductance  $L_1$  is given as

$$L_1 = -|L_2| \quad \text{with} \quad |L_1| < |L_2|$$

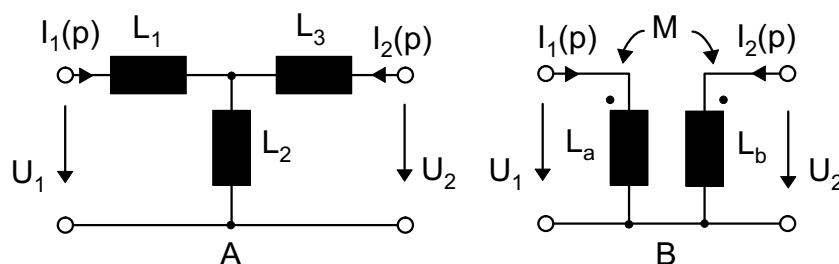The two-port A should be replaced by the ideal transformer B. There the primary inductance  $L_a$  is coupled to the secondary inductance  $L_b$  by  $M^2 = L_a \cdot L_b$ .



- 1.13.1 Determine the impedance matrices  $\vec{Z}_A$  and  $\vec{Z}_B$  of the two-ports.
- 1.13.2 Determine the dependence  $L_3 = f(L_1, L_2)$  which is necessary for the equivalence of the two-ports.
- 1.13.3 With the result of 1.13.2 determine  $M$ ,  $L_a$  and  $L_b$  as functions of  $L_1$  and  $L_2$ , in order to replace the two-port A by the two-port B.

**Problem 1.14**

The impedances  $Z_a$  and  $Z_b$  of a symmetric bridge two-port (as shown in figure 1.20 of the manuscript) are given by

$$Z_a = \frac{R_1}{pR_1C_1 + 1} \quad \text{and} \quad Z_b = \frac{pR_2C_2 + 1}{pC_2} \quad \text{with } R_2 > R_1$$

- 1.14.1 Draw the realisations of  $Z_a$  and  $Z_b$  using passive RLC-elements and denote the components.
- 1.14.2 Draw the symmetric bridge two-port.
- 1.14.3 Using the BARTLETT' symmetry proposition, derive from the symmetric bridge two-port of 1.14.2 an equivalent two-port with a symmetrical structure without crossing branches.

**Chapter 2**  
**Characteristics and realization**  
**of passive two-terminal**  
**network function**

**Problem 2.1**

Given is the normalised impedance function

$$Z_n(\rho) = \frac{3\rho^4 + 8\rho^2 + 1}{\rho^3 + \rho} \quad \text{with} \quad \rho = \varsigma + j\Omega$$

- 2.1.1 Determine the poles and zeros of  $Z_n(\rho)$  and sketch them in a pole-zero-diagram.
- 2.1.2 Is it possible to implement the impedance function  $Z_n(\rho)$  (after de-normalisation) using passive elements? Why or why not?
- 2.1.3 Expand  $Z_n(\rho)$  into a series of partial fractions and draw the corresponding circuit, naming the components.

**Problem 2.2**

The description of a fully normalised impedance function  $Z_n(\rho)$  of a passive two-pole as a partial fraction is

$$Z_n(\rho) = \frac{a_0}{\rho} + \sum_{\nu=1}^N \frac{2a_\nu \rho}{\rho^2 + \Omega_\nu^2} + a_\infty \rho$$

with  $a_0$ ,  $a_\nu$ ,  $a_\infty$  real and positive.

- 2.2.1 Show that  $Z_n(\rho = j\Omega)$  is an imaginary function in  $\Omega$  and that the gradient of  $\text{Im}\{Z_n(j\Omega)\}$  is always positive, i.e.

$$\frac{\partial}{\partial \Omega} \text{Im}\{Z_n(j\Omega)\} > 0 \quad \forall \quad \Omega$$

**Problem 2.3**

Given is the following normalised impedance function of a two-pole

$$Z_n(\rho) = \frac{8\rho^4 + 80\rho^2 + 72}{\rho^3 + 4\rho}$$

- 2.3.1 Determine the poles and zeros of  $Z_n(\rho)$  and draw the corresponding pole-zero-plot.
- 2.3.2 Which kind of two-pole is described by  $Z_n(\rho)$ ?
- 2.3.3 Expand  $Z_n(\rho)$  into a sum of partial fractions and draw the corresponding circuit, naming the components.
- 2.3.4 Denormalise  $Z_n(\rho)$  using

$$R_N = 100 \, \Omega \quad \text{and} \quad \omega_N = 10^4 \, \text{s}^{-1}$$

and draw the corresponding network.

**Problem 2.4**

Analyse if the given normalised two-pole impedance functions describe passive LC-Transformer two-poles and justify your answer.

$$Z_{n1}(\rho) = \frac{\rho^2 + 3\rho + 1}{\rho}$$

$$Z_{n2}(\rho) = \frac{\rho^3}{(\rho^2 + 2)^2}$$

$$Z_{n3}(\rho) = \frac{(\rho^2 + 2)(\rho^2 + 4)}{\rho^2 + 8}$$

$$Z_{n4}(\rho) = \frac{\rho}{\rho^2 + 3}$$

$$Z_{n5}(\rho) = \frac{2\rho^4 + 11\rho^2 + 4}{\rho^3 + 4\rho}$$

$$Z_{n6}(\rho) = \frac{\rho + 2}{\rho^3 + 1}$$

**Problem 2.5**

Given is the following normalised impedance function.

$$Z_n(\rho) = \frac{24\rho^3 + 192\rho}{\rho^4 + 20\rho^2 + 64} \quad \text{with} \quad \rho = \frac{p}{\omega_N} = \varsigma + j\Omega$$

2.5.1 Determine the poles and zeros of  $Z_n(\rho)$  and draw the corresponding pole-zero-plot.

2.5.2 Calculate and draw the implementation of the

- 1st Foster-Structure
- 2nd Foster-Structure
- 1st Cauer-Structure
- 2nd Cauer-Structure

**Problem 2.6**

Given is the following normalised impedance function.

$$Z_n(\rho) = \frac{\rho^2 + 8\rho + 12}{\rho^2 + 4\rho}$$

- 2.6.1 Which type of two-pole is described by  $Z_n(\rho)$ , justify your answer.
- 2.6.2 Calculate the corresponding continued fraction arrangement, which can be obtained by subtracting the poles at  $\rho = \infty$ . I.e. the 1st Cauer-Form.
- 2.6.3 Calculate the corresponding admittance-partial-fraction arrangement, i.e. the 2nd Foster-Form.
- 2.6.4 De-normalise the impedance-function  $Z_n(\rho)$  using the normalised resistance and frequency

$$R_N = 100 \Omega \quad \text{and} \quad \omega_N = 10^4 \text{ s}^{-1}$$

and draw the network found in 2.6.3 with de-normalised elements.

**Problem 2.9**

Given is the following normalised impedance function of a passive RC-two-pole.

$$Z_n(\rho) = \frac{\rho^2 + 4\rho + 3}{\rho^2 + 2\rho} \quad \text{with} \quad \rho = \frac{p}{\omega_N} = \varsigma + j\Omega$$

and

$$\omega_N = 10^3 \text{ s}^{-1} \quad \text{and} \quad R_N = 100 \text{ } \Omega$$

- 2.9.1 Determine the linear-factor-description of  $Z_n(\rho)$ .
- 2.9.2 Determine the poles and zeros of  $Z_n(\rho)$  and draw the corresponding pol-zero-plot.
- 2.9.3 Develop the impedance-partial-fraction-description (the 1st Forster-Form) of  $Z_n(\rho)$ .
- 2.9.4 Draw the corresponding circuit with the normalised components and their values.
- 2.9.5 De-normalise the component-values found in 2.9.4 and give their resistance in Ohm and the capacitance in  $\mu\text{F}$ .



**Chapter 3**  
**Characteristics and realisation**  
**of active RC-two-ports**  
**network function**

**Problem 3.1**

For an active 2nd order RC-high-pass, realised with the 'method of infinite gain and single feed-back path', one can describe the system function as follows:


$$H_L(p) = - \frac{\frac{C_{1A} \cdot C_{2A}}{C_{1B} \cdot (C_{1A} + C_{2A})} \cdot p^2}{p^2 + \frac{G_{1B} + G_{2B}}{C_{2B}} \cdot p + \frac{G_{1B} \cdot G_{2B}}{C_{1B} \cdot C_{2B}}}$$

3.1.1 Determine the fully normalised function  $H_{Ln}(\rho)$  of  $H_L(p)$ .

3.1.2 Determine the normalised resistances and capacitances of the active high-pass-circuit as a function of the normalised cut-off frequency  $\Omega_g = \omega_g/\omega_N$  and the constants  $H_0$  and  $b$ .

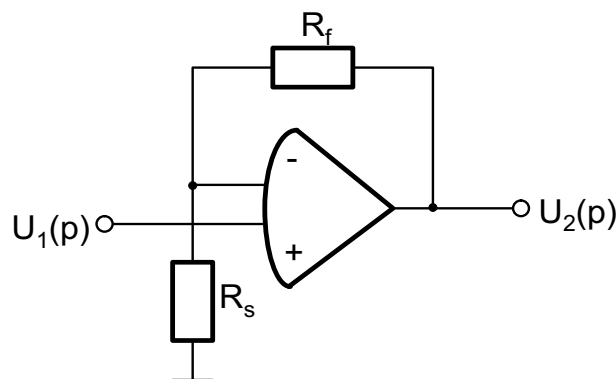**Problem 3.2**


Given is the following circuit, constituted by an ideal operational amplifier and two resistances:



3.2.1 Determine the system function  $H_L(p) = U_2(p)/U_1(p)$ .

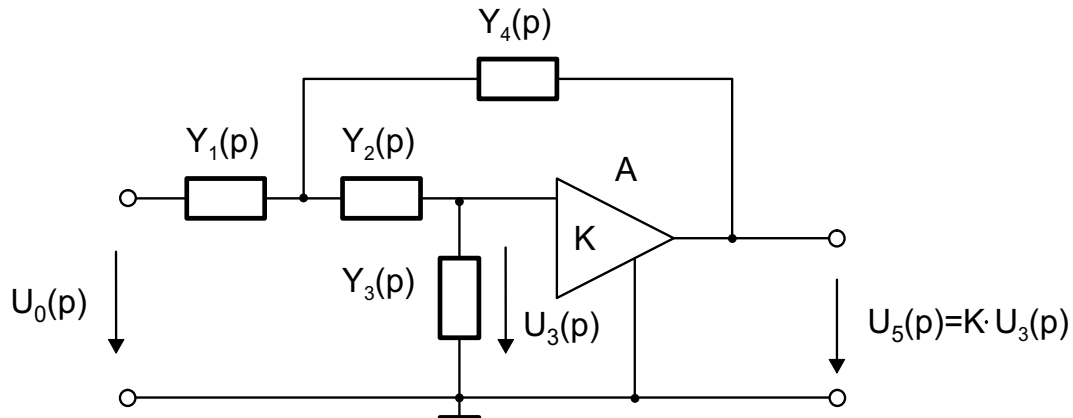**Problem 3.3**


Given is the following circuit with the active voltage-driven voltage-source A (input impedance  $Z_e \rightarrow \infty$ ):



- 3.3.1 Determine the system function  $H_L(p) = U_5(p)/U_0(p)$  as a function of  $Y_1(p)$ ,  $Y_2(p)$ ,  $Y_3(p)$ ,  $Y_4(p)$  and  $k$ .
- 3.3.2 Determine the system function  $H_L(p)$  for the case that  $Y_1(p)$  is the admittance of a resistor  $R_1$ ,  $Y_2(p)$  is the admittance of a resistor  $R_2$ ,  $Y_3(p)$  is the admittance of a capacitor with the capacitance  $C_3$  and  $Y_4(p)$  is the admittance of a capacitor with the capacitance  $C_4$ .
- 3.3.3 Which kind of filter is described by the circuit shown in 3.3.2?
- 3.3.4 Determine the input impedance  $Z_e = U_0(p)/I_1(p)$  of the circuit as a function of the admittances  $Y_1(p)$ ,  $Y_2(p)$ ,  $Y_3(p)$ ,  $Y_4(p)$  and the constant  $k$ .

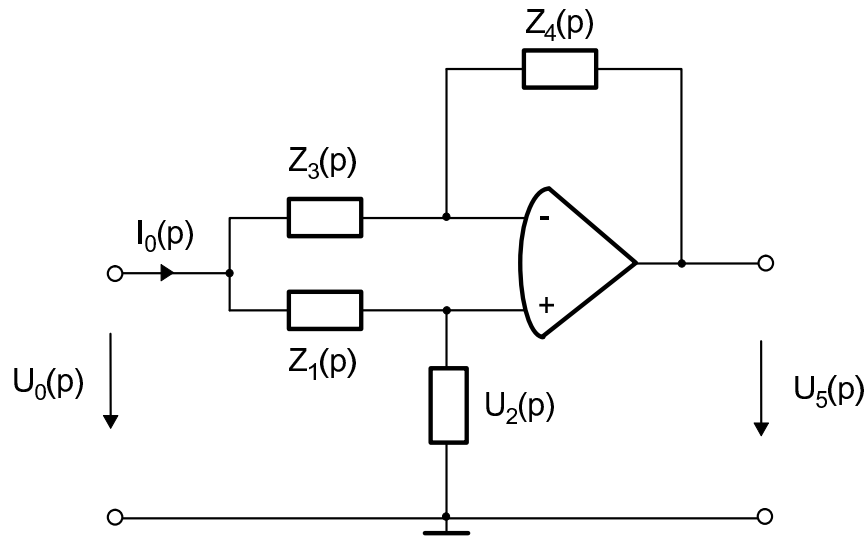**Problem 3.4**

Given is the following circuit with the ideal operational amplifier:



- 3.4.1 Determine the system function  $H_L(p) = U_5(p)/U_0(p)$  as a function of the impedances  $Z_1(p)$ ,  $Z_2(p)$ ,  $Z_3(p)$  and  $Z_4(p)$ ; and also as a function of the admittances  $Y_1(p)$ ,  $Y_2(p)$ ,  $Y_3(p)$ , and  $Y_4(p)$ .
- 3.4.2 Determine the input impedance  $Z_e(p) = U_0(p)/I_0(p)$ .
- 3.4.3 The impedances  $Z_1(p)$ ,  $Z_2(p)$ ,  $Z_3(p)$  and  $Z_4(p)$  shall be the impedances of resistors or capacitors. Draw a circuit constituted by these elements, which describes a 1st order active allpass.